

Microprocessor Systems Laboratory

Lab Assignment 1



23.09.2022

Lab Assignment 1- session 2

- Previous session:
 - Got started with LogiSim
 - Designed components for an ALU and a controller:
 - Subtractor (Half, full)
 - Comparator
 - Decoder (4x2)
 - Encoder (2x4)
 - MUX (4x1)


Lab Assignment 1- session 2

 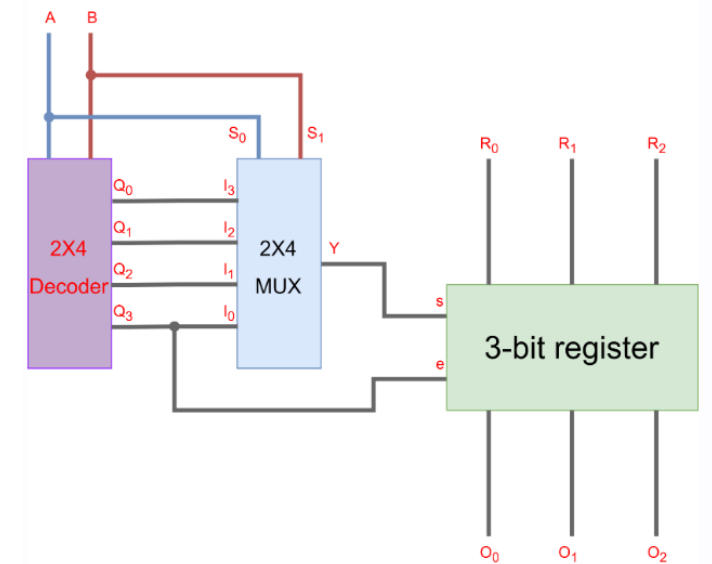- This session:
 - Finish parts 1 and 2
 - Write the truth tables in a document file
 - Save each component separately
 - Start part 3-section 1:
 - Do Home Task 1, part 1, consider it as a Flip-Flop
 - Use it as FF for designing a 3-bit register




Lab Assignment 1- session 3

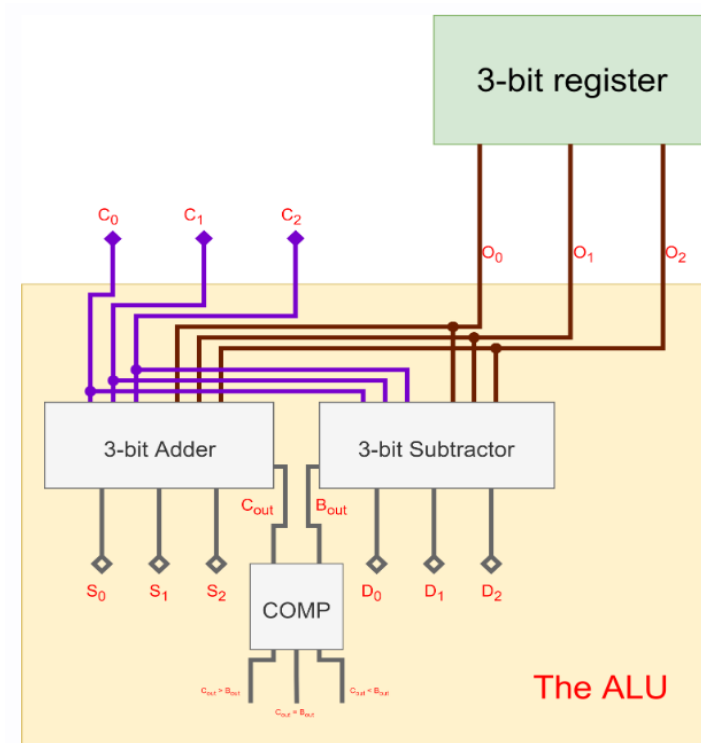- This session:
 - Complete the part 3-section 1
 - Create the designs for part 3-section 2:





group1 (IASM)

 

group2 (MAHM)

3-bit Full Adder and Subtractor

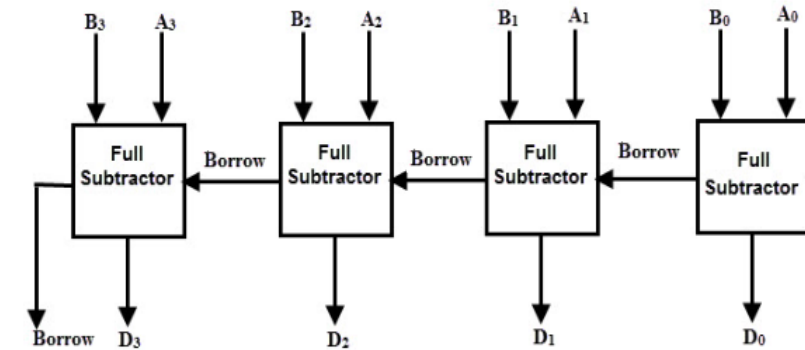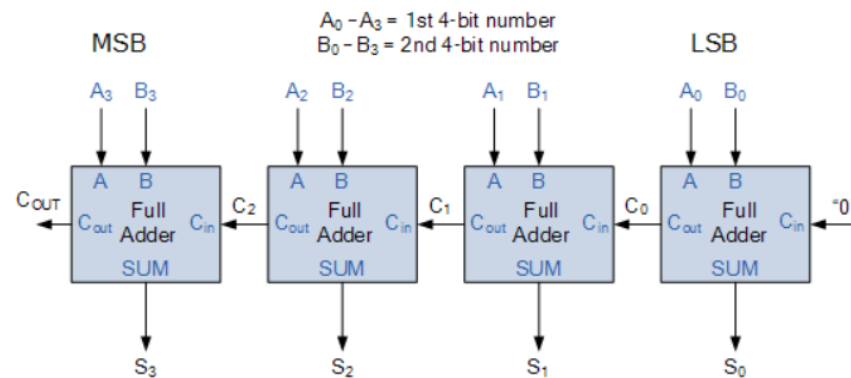- Full Adder:
 - $S = (A \text{ XOR } B) \text{ XOR } C_{in}$
 - $C_{out} = (A \text{ AND } B) \text{ OR } (A \text{ AND } C_{in}) \text{ OR } (B \text{ AND } C_{in})$
- You have to create a 3-bit adder
- You have to create a 3-bit subtractor





TAL TECH

THANKS FOR YOUR ATTENTION