

# Power Electronics

## Lecture 2

### BUCK converter

01

Voltage regulator

02

Derivation of the buck converter

03


Converter operation in CCM and DCM

04

Buck converter characteristics
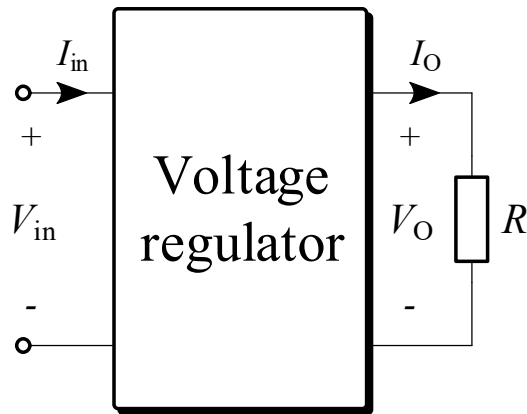
# Voltage regulator


**Voltage regulator** maintains the constant output voltage  $V_O$  regardless the input voltage  $V_{in}$  and the output current  $I_O$



In an ideal lossless voltage regulator  $P_{in} = P_O$

$$P_{in} = P_O \Rightarrow V_{in} \times I_{in} = V_O \times I_O$$

$$I_{in} = I_O \frac{V_O}{V_{in}}$$

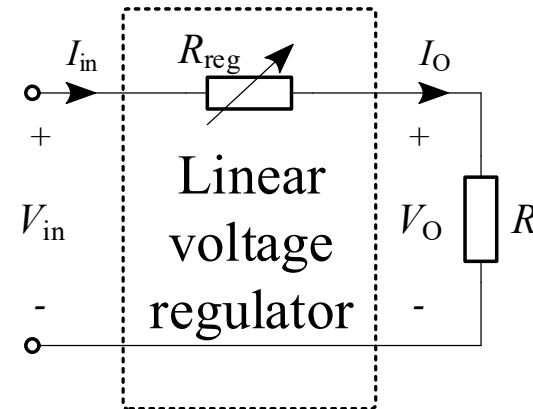

In a linear regulator  $I_{in} = I_O$  and  $V_{in} = V_O + I_O R_{reg}$


$$P_{in} = V_{in} \times I_{in} = (I_O R_{reg} + V_O) \times I_O = I_O^2 R_{reg} + V_O \times I_O = I_O^2 R_{reg} + P_O$$

A linear regulator is not an ideal because great amount of energy is lost on  $R_{reg}$ .
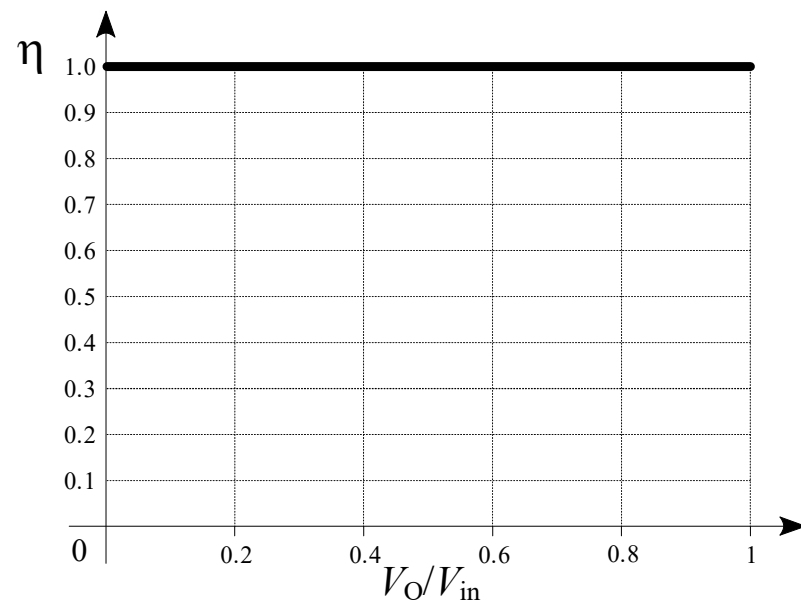
# Efficiency of ideal and linear regulators


Efficiency of an ideal regulator

$$P_{in} = P_o$$
$$\eta = \frac{P_o}{P_{in}} = 1$$




Efficiency of a linear regulator
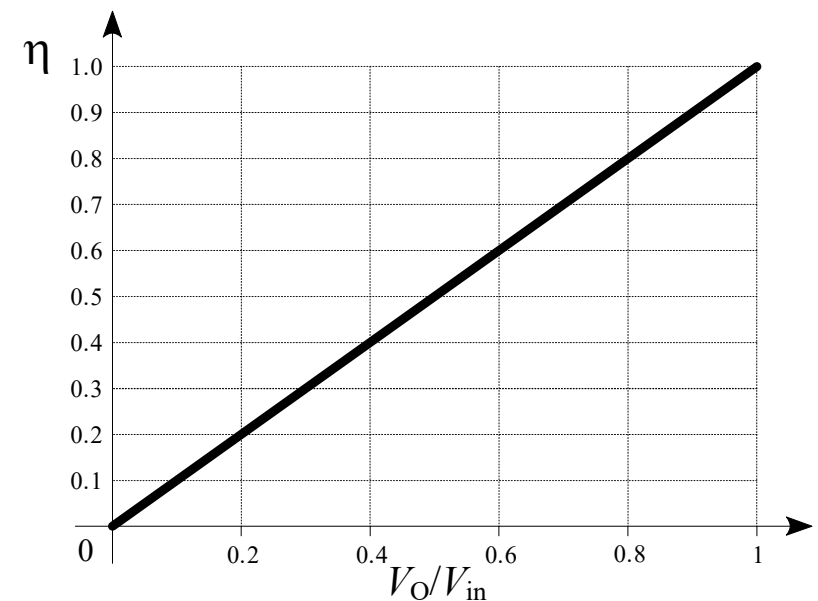
$$P_{in} \neq P_o$$
$$\eta = \frac{P_o}{P_{in}} = \frac{V_o \times I_o}{V_{in} \times I_{in}} \stackrel{I_{in}=I_o}{=} \frac{V_o}{V_{in}}$$



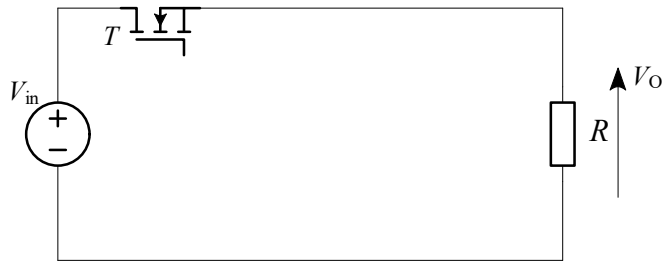
# Derivation of BUCK converter topology in four steps

Applying the switch  $T$  increases the efficiency




The output voltage is rectangular but not constant

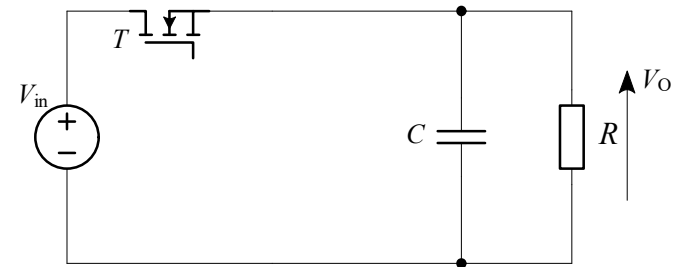The output capacitor  $C$  keeps the voltage constant




Capacitors should not be connected directly to voltage sources

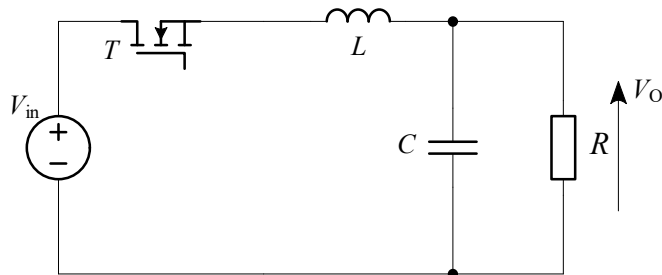The inductor  $L$  interconnects the capacitor and  $V_{in}$



The switch should not disconnect the inductor current

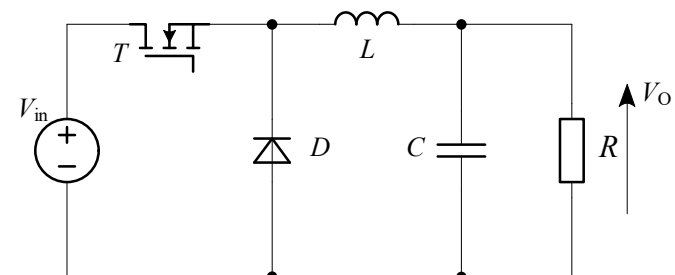
Diode protects the switch against voltage surge




BUCK converter topology also known as step down converter
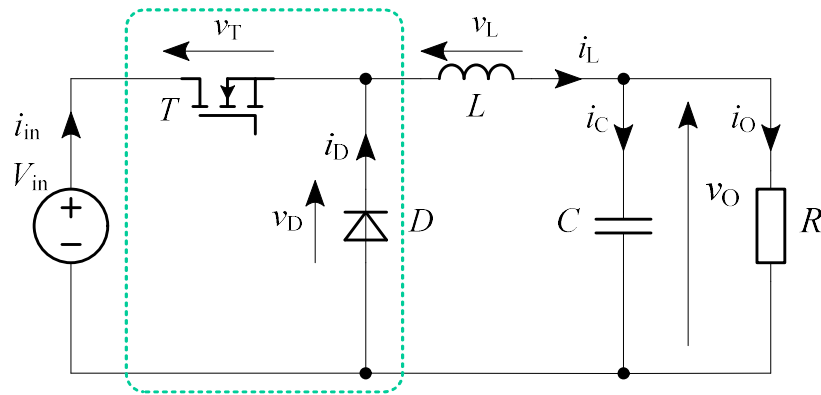
# Buck converter

The buck converter (a step-down converter) utilizes **switching power block**




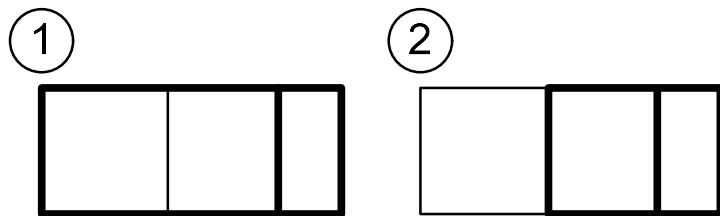Transistor  $T$  works in on- and off-state which corresponds to two equivalent circuits (with marked current paths)




Inductor voltage allows to determine the inductor current which is one of the buck converter state variable.

In steady state operation:

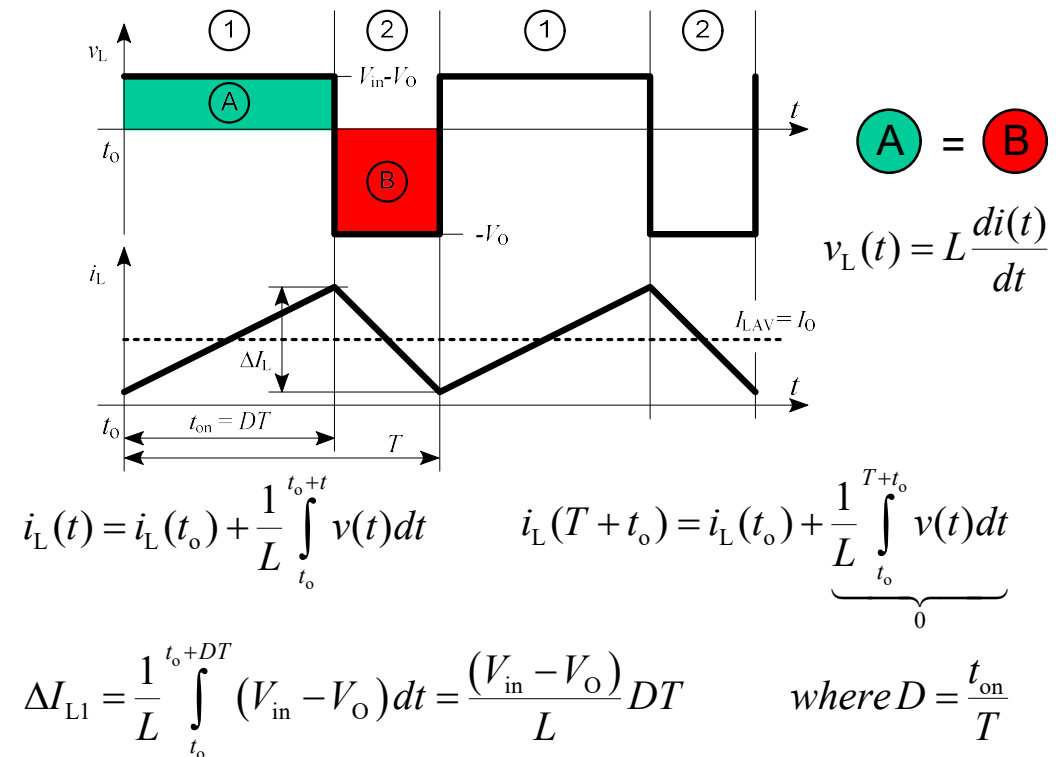

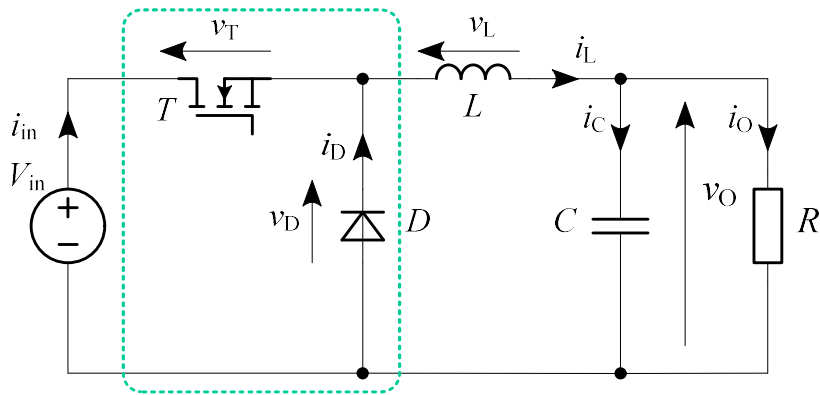
# Buck converter


The buck converter (a step-down converter) utilizes **switching power block**



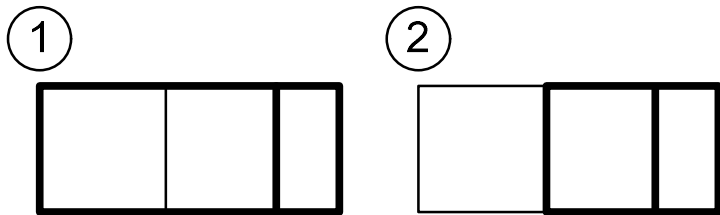
Transistor  $T$  works in on- and off-state which corresponds to two equivalent circuits (with marked current paths)



Operation not in steady state:

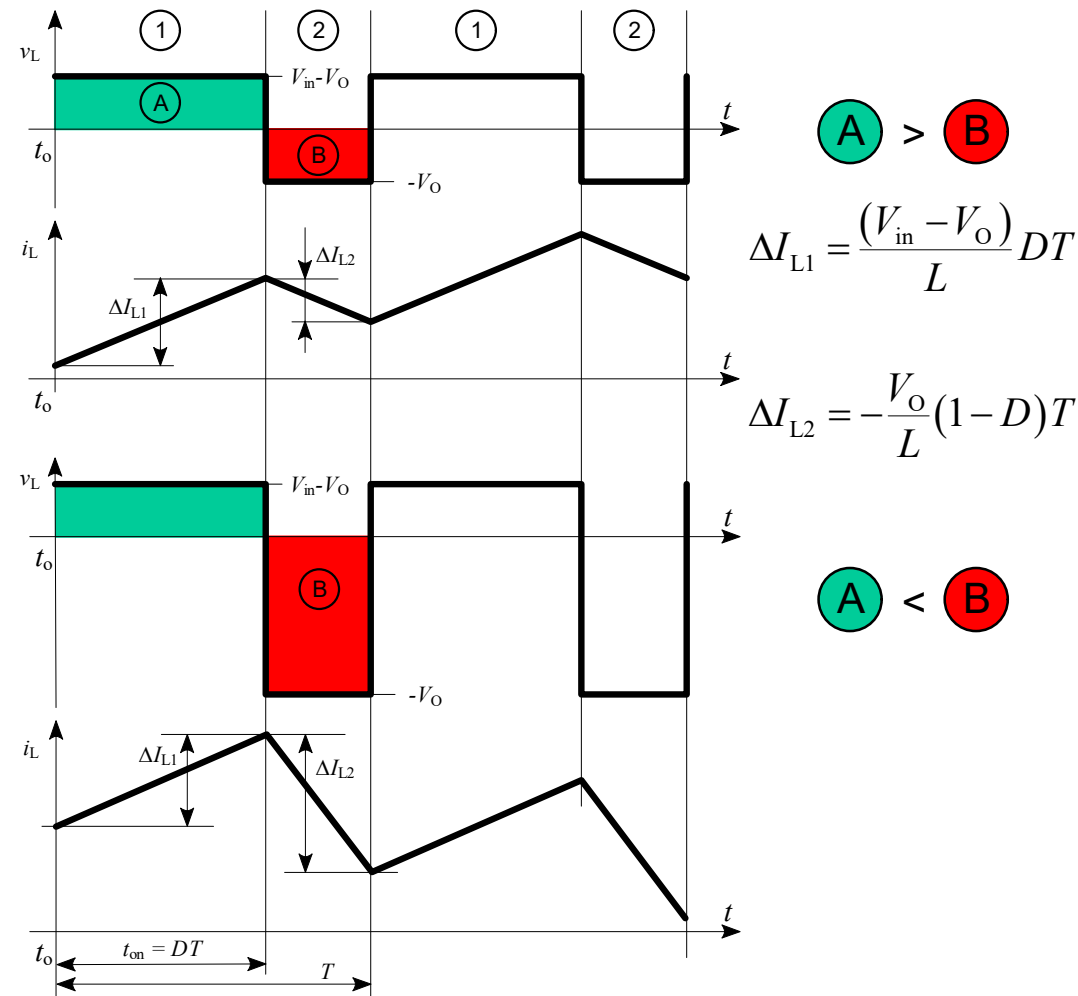

# Capacitor current and voltage

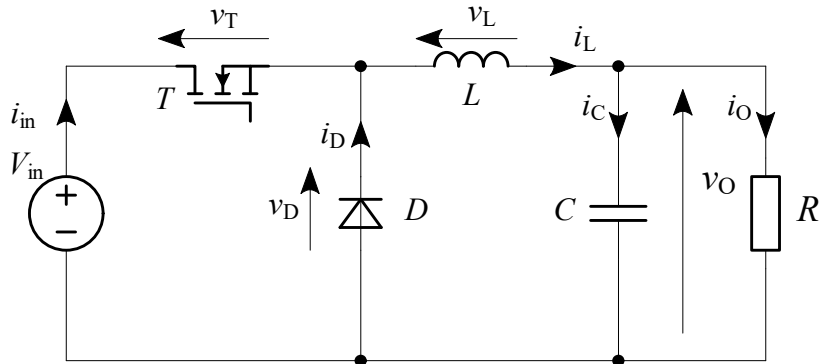


The capacitor current is given as  $v_o(t) = v_o(t_o) + \frac{1}{C} \int_{t_o}^{t_o+t} i_C(t) dt$

which leads to  $v_o(T + t_o) = v_o(t_o) + \frac{1}{C} \int_{t_o}^{T+t_o} i_C(t) dt$

Which means that capacitor current in the periodic steady state has the average value equal to zero

$$I_{CAV} = \frac{1}{T} \int_{t_o}^{T+t_o} i_C(t) dt = 0$$


Operation in steady state:

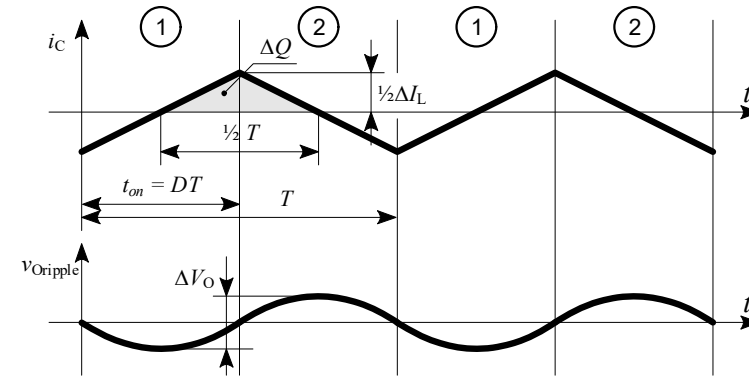

$$\begin{aligned} \Delta Q &= \frac{1}{2} \cdot \frac{T}{2} \cdot \frac{\Delta I_L}{2} = \\ &= \frac{T \Delta I_L}{8} = \frac{\Delta I_L}{8f} = \\ &= \frac{V_{in} - V_o}{8f^2 L} D \end{aligned}$$

$$Q_1 > Q_2$$

Operation not in steady state:

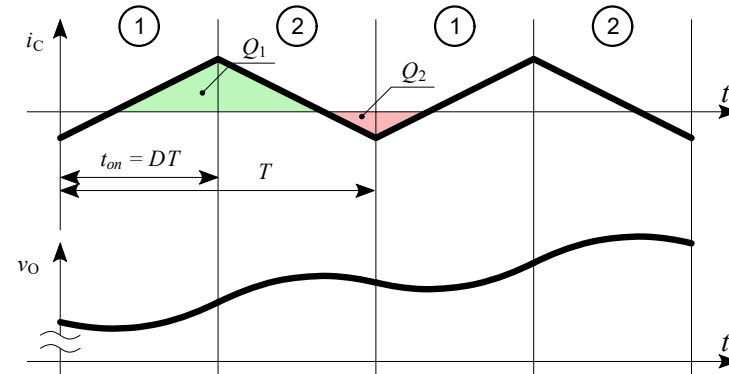


$$\begin{aligned} \Delta V_o &= \frac{\Delta Q}{C} = \\ &= \frac{V_{in} - V_o}{8f^2 LC} D = \\ &= \frac{V_{in} D (1 - D)}{8f^2 LC} \end{aligned}$$

The output voltage increases
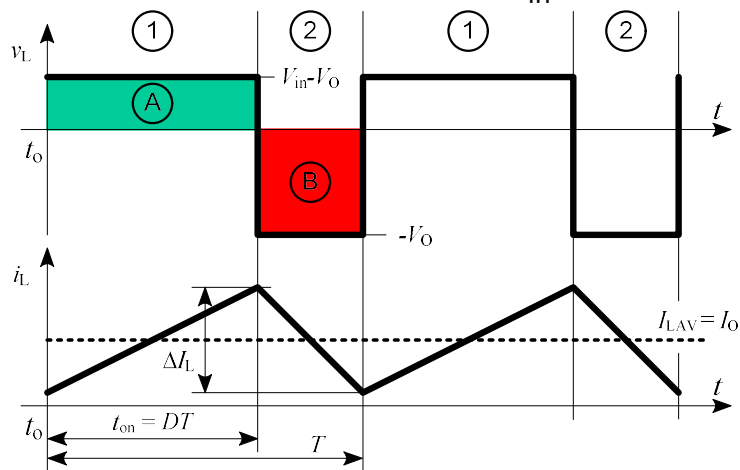
# The output voltage

Due to the inductor voltage is zero in a steady state it is possible to derive the output voltage as a function of duty cycle  $D$  and input voltage  $V_{in}$ .



$$\text{Area}_A - \text{Area}_B = 0$$

$$(V_{in} - V_O)DT - V_O(1-D)T = 0$$

$$V_{in}D - \underline{V_O D} - V_O + \underline{V_O D} = 0$$


$$V_{in}D - V_O = 0$$

$$\boxed{V_O = V_{in}D}$$

The output voltage  $V_O = V_{in}D$  is only true when the converter works in continuous conduction mode CCM

The output voltage control characteristic

$$\frac{V_O}{V_{in}} = D$$

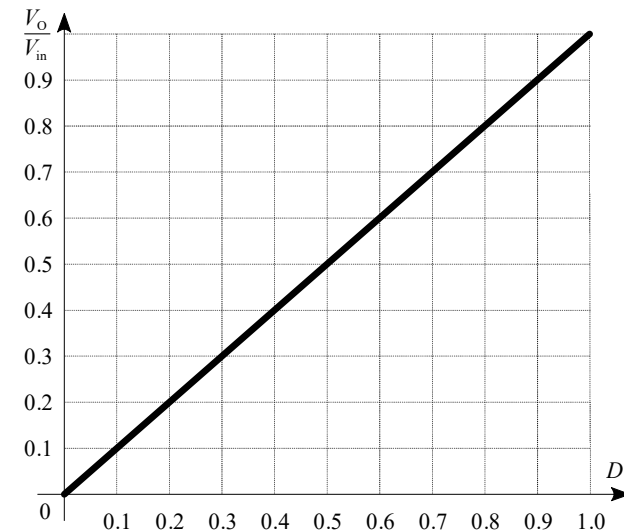



# CCM operation

Continuous conduction mode (CCM) means that the converter operates with the continuous inductor current



Inductor current ripple is given as:

$$\Delta I_L = \frac{1}{L} \int_0^{DT} v_L(t) dt = \frac{V_{in} - V_O}{L} DT$$

$$\Delta I_L = \frac{V_O = V_{in} D}{L} D(1-D)$$

$$\Delta I_L = \frac{V_O T}{L} (1-D) = \frac{V_{in} T}{L} D(1-D)$$

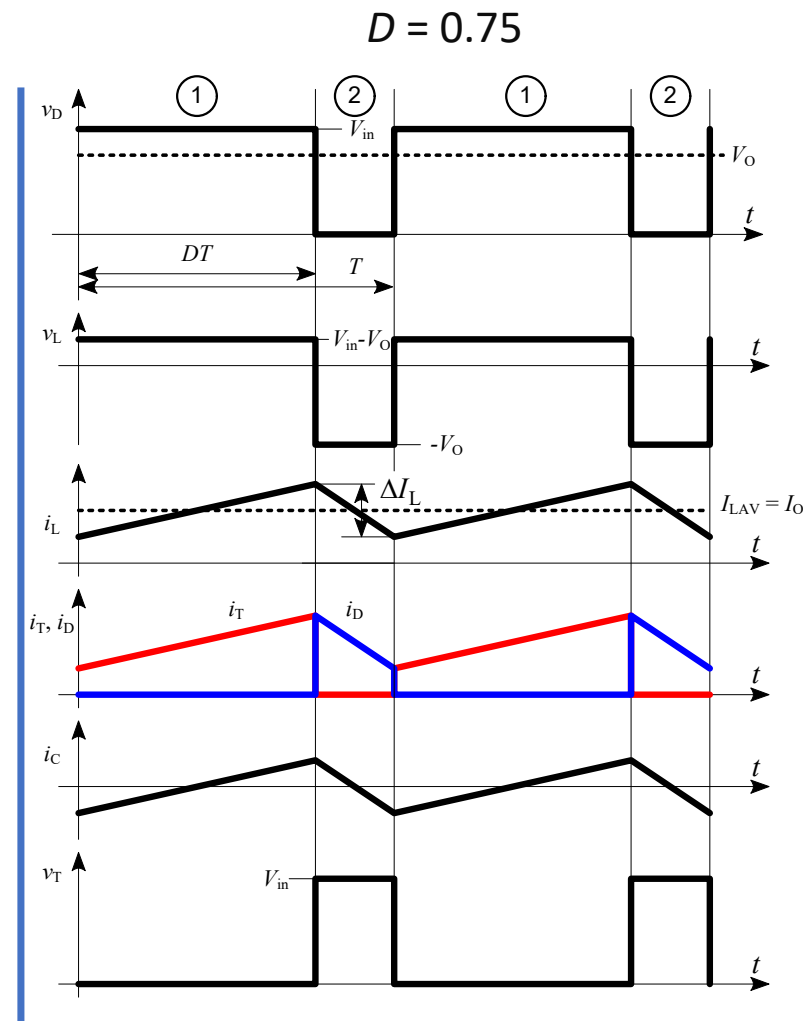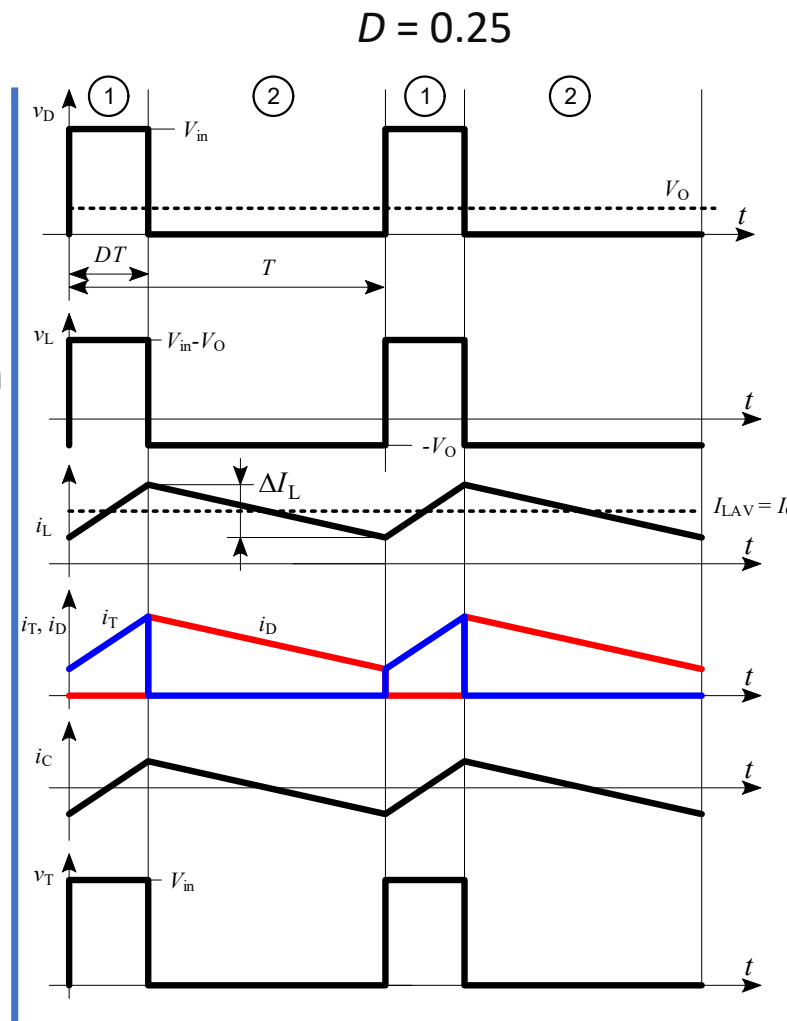It is assumed that the output voltage ripples are zero






# CCM/DCM boundary

When the output current  $I_O = I_{Ocrit} = \frac{1}{2}\Delta I_L$  the converter operates at boundary between continuous conduction mode (CCM) and discontinuous conduction mode (DCM)




$$I_{Ocrit} = \frac{1}{2}\Delta I_L = \frac{V_{in}T}{2L}D(1-D)$$

$$I_{Ocrit} = I_{ref}D(1-D)$$

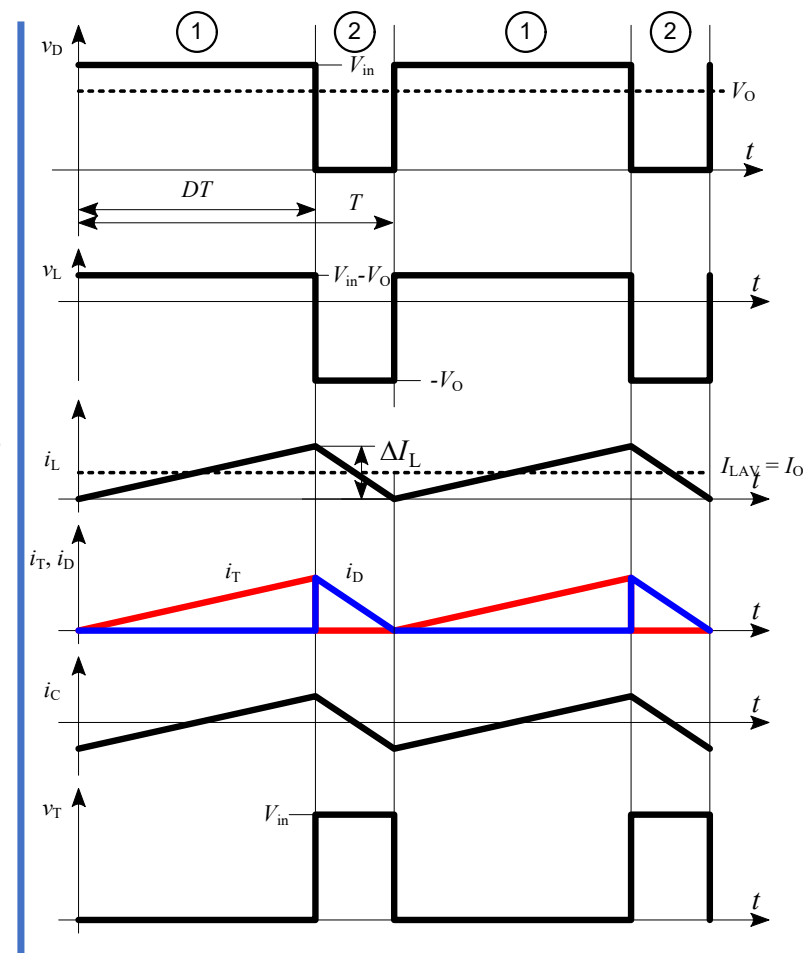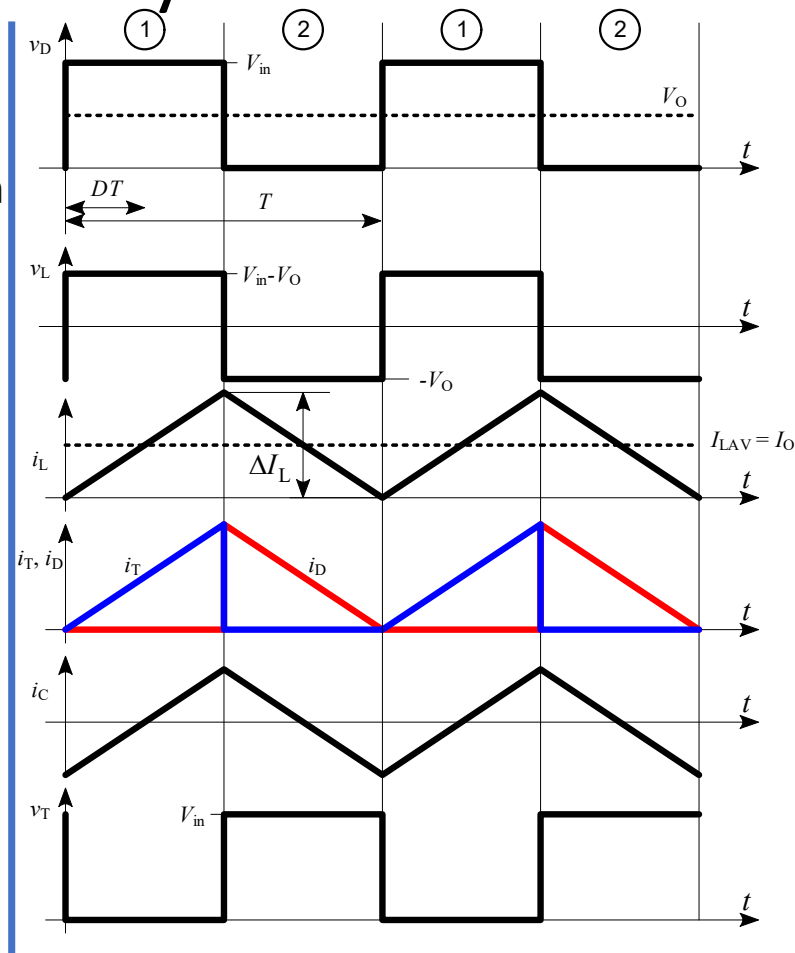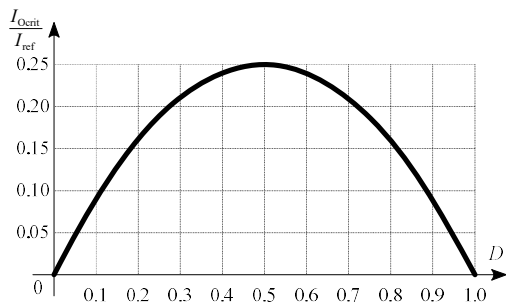
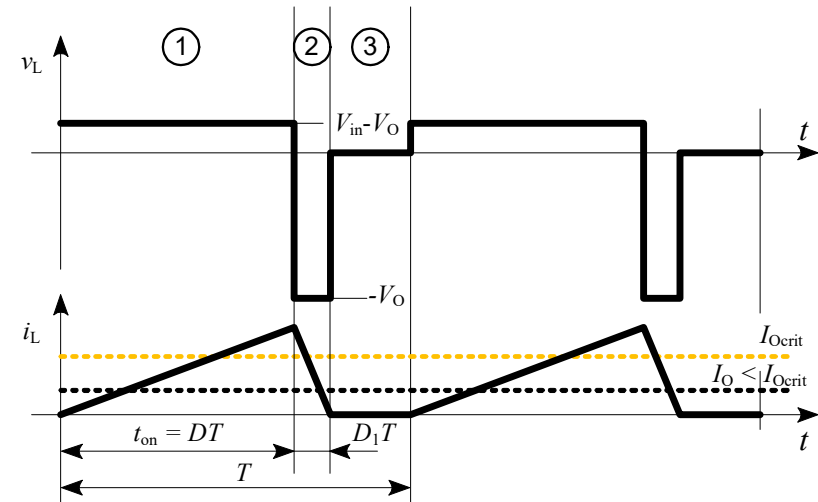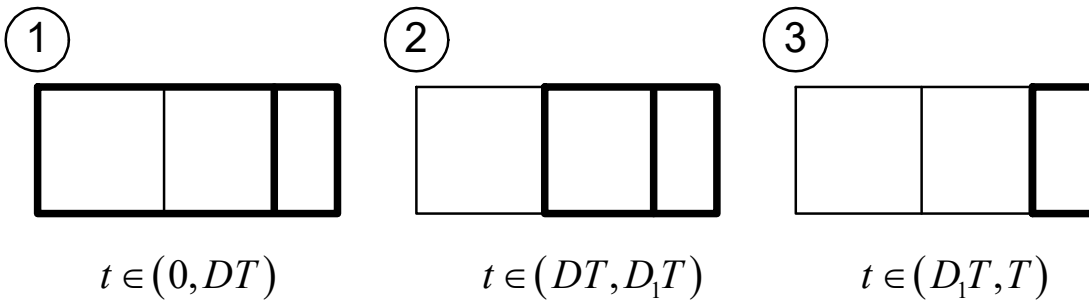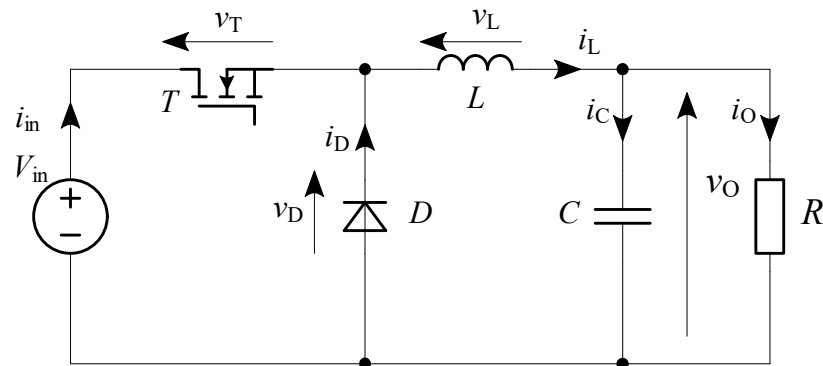
# DCM operation

When the output current  $I_O < I_{Ocrit}$  the converter operates in discontinuous conduction mode (DCM)



$$V_{LAV} = (V_{in} - V_O)D + (-V_O)D_1 = 0$$

$$D_1 = \frac{V_{in} - V_O}{V_O} D$$

$$I_O = \frac{1}{2} \Delta I_L (D + D_1), \text{ where } \Delta I_L = \frac{V_{in} - V_O}{L} DT$$

$$I_O = \frac{1}{2} \frac{V_{in} - V_O}{L} DT \left( D + \frac{V_{in} - V_O}{V_O} D \right) = \frac{V_{in} - V_O}{2L} TD^2 \left( 1 + \frac{V_{in} - V_O}{V_O} \right)$$

$$I_O = \frac{V_{in} - V_O}{2L} TD^2 \left( \frac{V_{in}}{V_O} \right)^{I_{ref} = \frac{V_{in} T}{2L}} = I_{ref} \frac{V_{in} - V_O}{V_O} D^2$$

# Output characteristics

In DCM the output voltage  $V_O$  is dependent on the output current  $I_O$ , input voltage  $V_{in}$  and duty cycle  $D$

$$I_O = I_{ref} \frac{V_{in} - V_O}{V_O} D^2 = I_{ref} \left( \frac{V_{in}}{V_O} - 1 \right) D^2$$

In DCM

$$\frac{I_O}{I_{ref}} \frac{1}{D^2} = \left( \frac{V_{in}}{V_O} - 1 \right) \Rightarrow \frac{V_{in}}{V_O} = \frac{I_O}{I_{ref}} \frac{1}{D^2} + 1$$


$$\frac{V_O}{V_{in}} = \frac{1}{\frac{I_O}{I_{ref}} \frac{1}{D^2} + 1}$$

In CCM

$$\frac{V_O}{V_{in}} = D$$

At CCM/DCM boundary

$$I_{Ocrit} = I_{ref} D(1 - D)$$

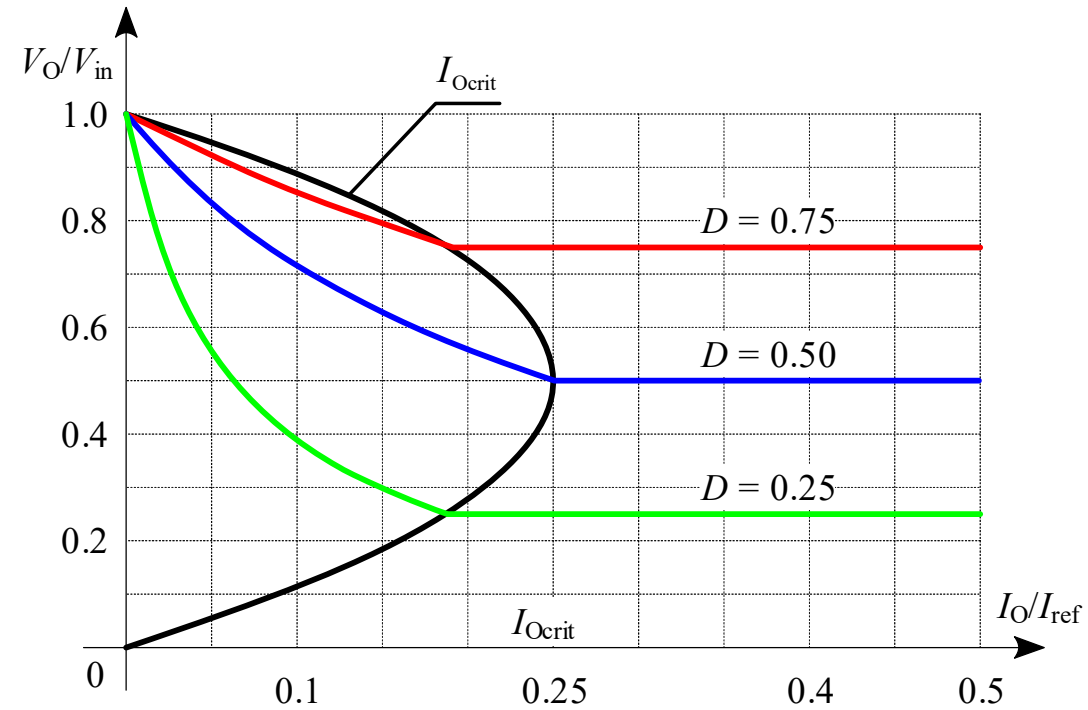

# Buck with $V_O = \text{const}$

$$I_O = \frac{V_{in} - V_O}{2L} T D^2 \left( \frac{V_{in}}{V_O} \right)^{I_{Oref} = \frac{V_O T}{2L}} = I_{Oref} (V_{in} - V_O) \frac{V_{in}}{V_O^2} D^2$$

In DCM

$$D^2 = \frac{\frac{I_O}{I_{Oref}}}{\left( \frac{V_{in}}{V_O} \right)^2 - \frac{V_{in}}{V_O}} \Rightarrow D = \sqrt{\frac{\frac{I_O}{I_{Oref}}}{\left( \frac{V_{in}}{V_O} \right)^2 - \frac{V_{in}}{V_O}}}$$


In CCM

$$D = \frac{V_O}{V_{in}}$$

At CCM/DCM boundary


$$I_{Ocrit} = \frac{V_{in} T}{2L} \frac{V_O}{V_O} D(1-D)$$
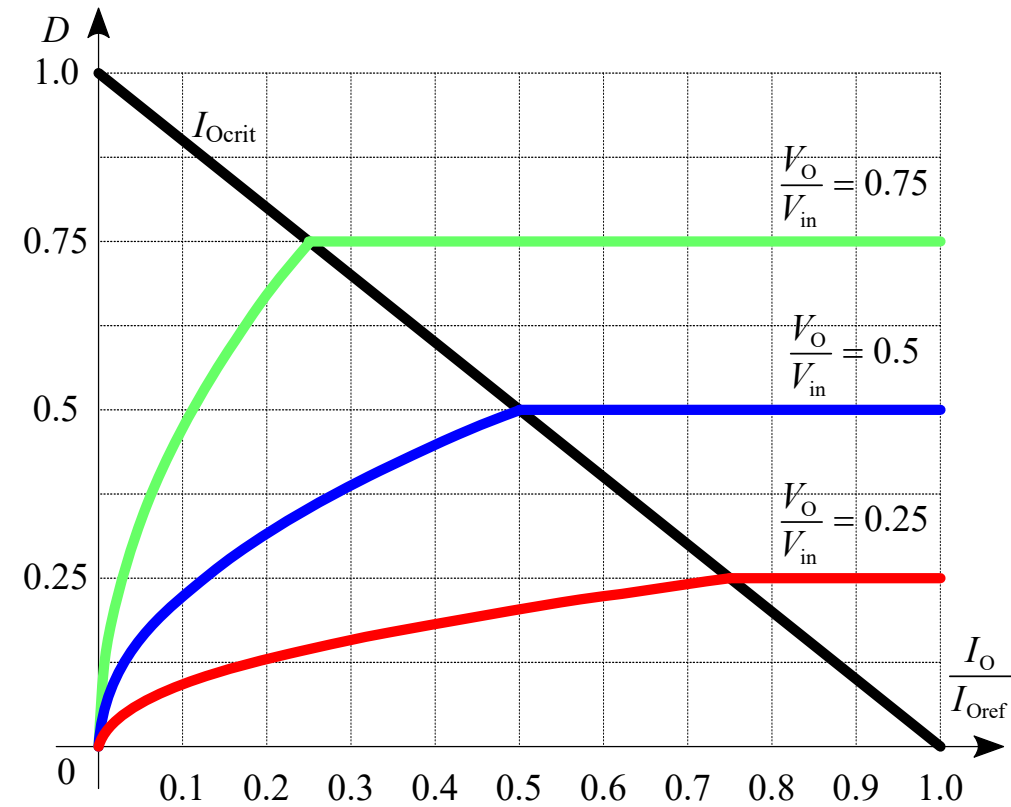
$$I_{Ocrit} = \frac{I_{Oref} = \frac{V_O T}{2L}}{I_{Oref} \frac{V_{in}}{V_O} D(1-D) = I_{Oref} \frac{1}{D} D(1-D) = I_{Oref} (1-D)}$$



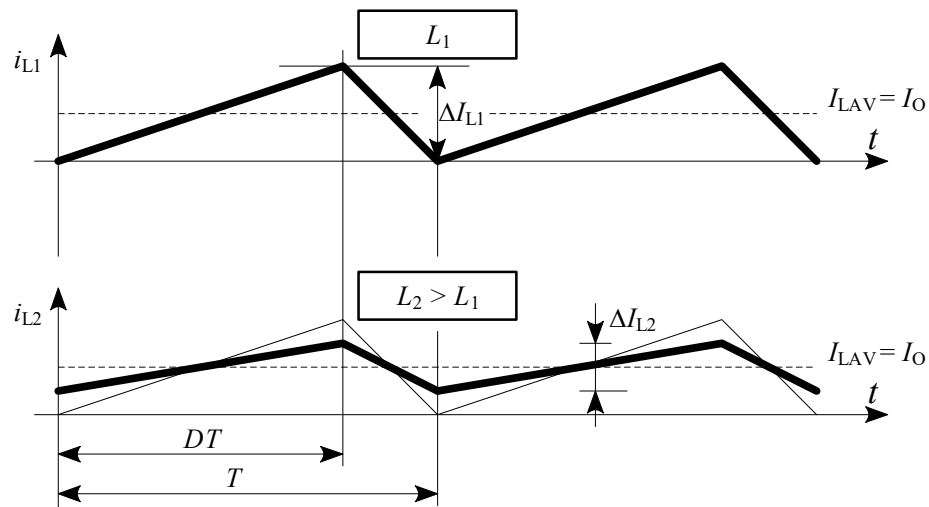
# Parameter influence

When the buck converter operates at DCM/CCM and inductance increases



The converter will work in CCM

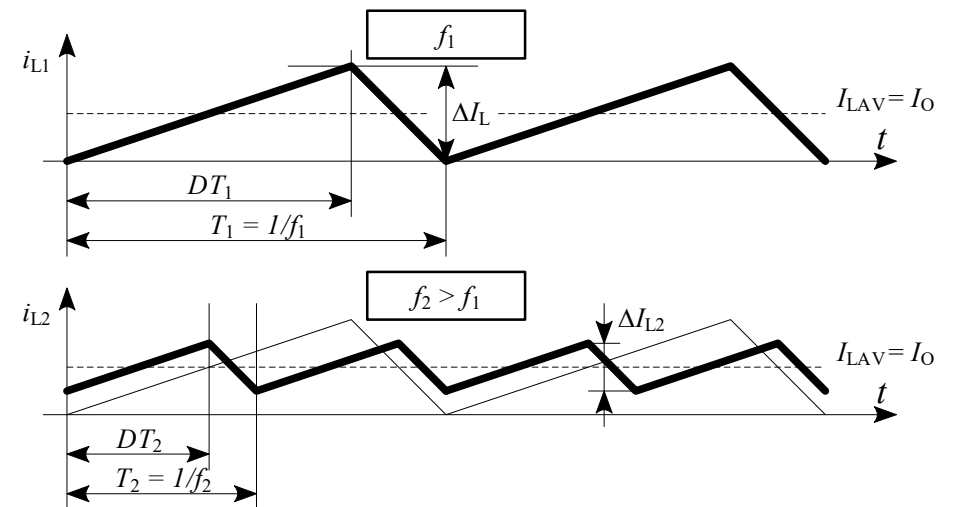When the buck converter operates at DCM/CCM and frequency increases



The converter will work in CCM