

Power Electronics

Lecture 5

Diode and thyristor rectifiers

01

Half wave diode and thyristor rectifier

02

Full wave rectifiers

03

Six pulse rectifiers



Half wave rectifiers

Half-wave rectifiers in practice are used most often in low-power applications.

The average current in the supply is not zero, this may cause problems in transformer performance.

Half-wave rectifiers are mainly analyzed because their operation is similar to more complicated circuits (like full-wave multipulse rectifiers).

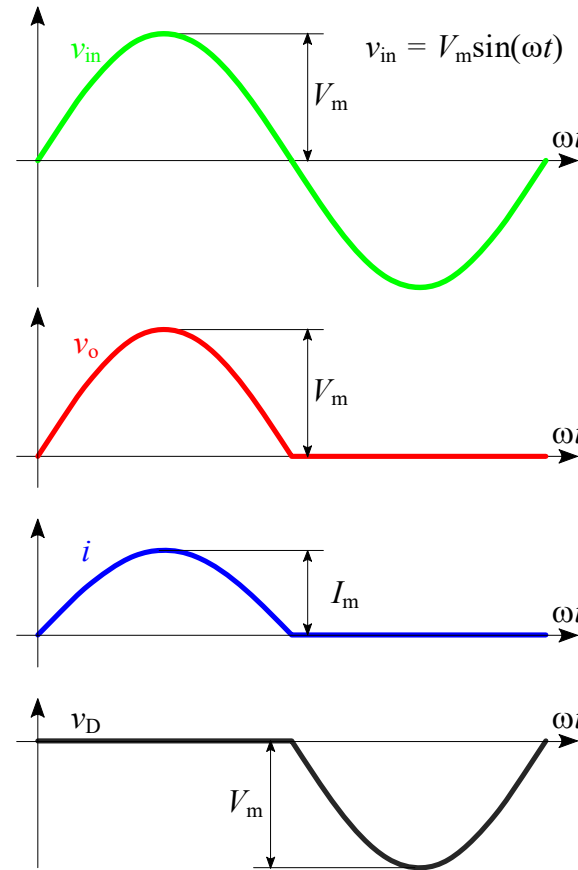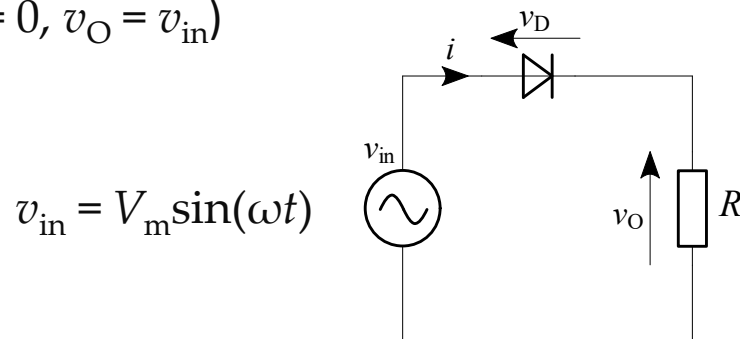In the half-wave diode rectifier with resistive load the current i flows when diode is forward biased ($v_{in} > 0$, $v_D = 0$, $v_O = v_{in}$)




$$v_o = \begin{cases} V_m \sin(\omega t) & \text{for } v_{in} > 0 \\ 0 & \text{for } v_{in} < 0 \end{cases}$$

$$i = \begin{cases} \frac{V_m}{R} \sin(\omega t) & \text{for } v_{in} > 0 \\ 0 & \text{for } v_{in} < 0 \end{cases}$$

$$v_D = \begin{cases} 0 & \text{for } v_{in} > 0 \\ -V_m \sin(\omega t) & \text{for } v_{in} < 0 \end{cases}$$

Half wave rectifiers

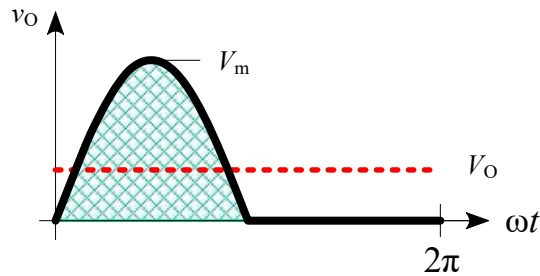The average value of the output voltage V_O is given as



$$V_O = \frac{1}{2\pi} \int_0^{\pi} V_m \sin(\omega t) d\omega t = -\frac{V_m}{2\pi} \left[\cos(\omega t) \right]_0^{\pi} = -\frac{V_m}{2\pi} [(-1) - 1] = \frac{V_m}{\pi}$$


The average value of the current

$$I_{AV} = \frac{V_O}{R} = \frac{V_m}{\pi R}$$

The rms value of the output voltage

$$V_{Orms} = \sqrt{\frac{1}{2\pi} \int_0^{\pi} [V_m \sin(\omega t)]^2 d\omega t} = \frac{V_m}{2}$$

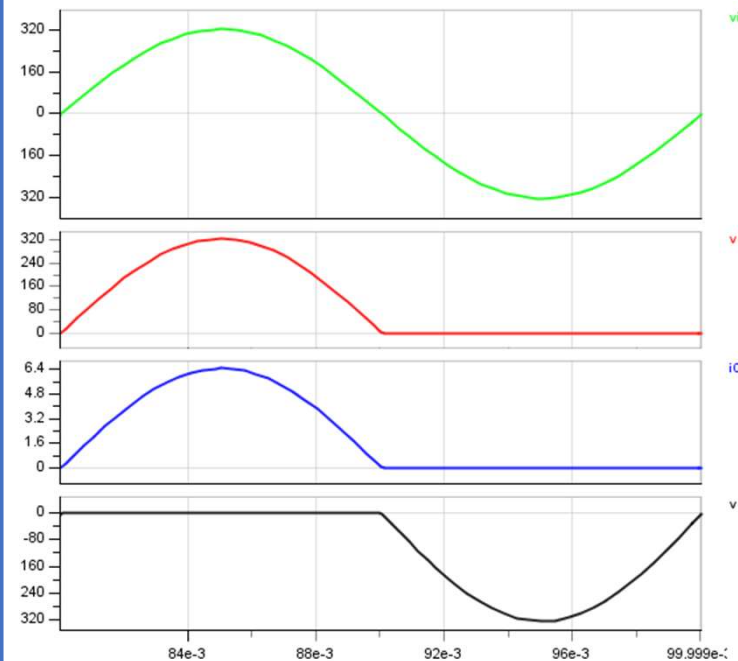Example of the diode half-wave diode rectifier with R load ($R = 50 \Omega$) supplied from sinusoidal voltage source $V_{inrms} = 230 \text{ V}$ ($V_m = 325 \text{ V}$).




Results

	avg	rms
vO	103.4488	162.4969
iO	2.069	3.2499
vD	-103.4488	162.4961
vin	-89.0743e-9	229.8053

Half wave rectifiers

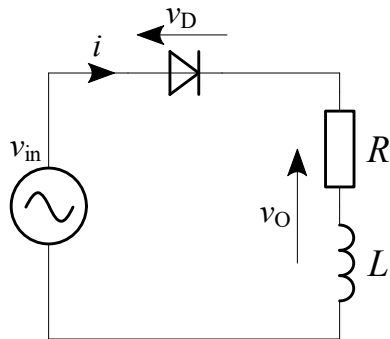
In the half-wave diode rectifier with resistive-inductive load the current i flows for positive input voltage and for a part when the input voltage is negative.



The current i is composed of two components, the forced response i_f and natural response i_n .

$$i = i_f + i_n = \underbrace{\frac{V_m}{Z} \sin(\omega t - \varphi)}_{i_f} + \underbrace{\frac{V_m}{Z} \sin(\varphi) e^{-\frac{t}{\tau}}}_{i_n}$$

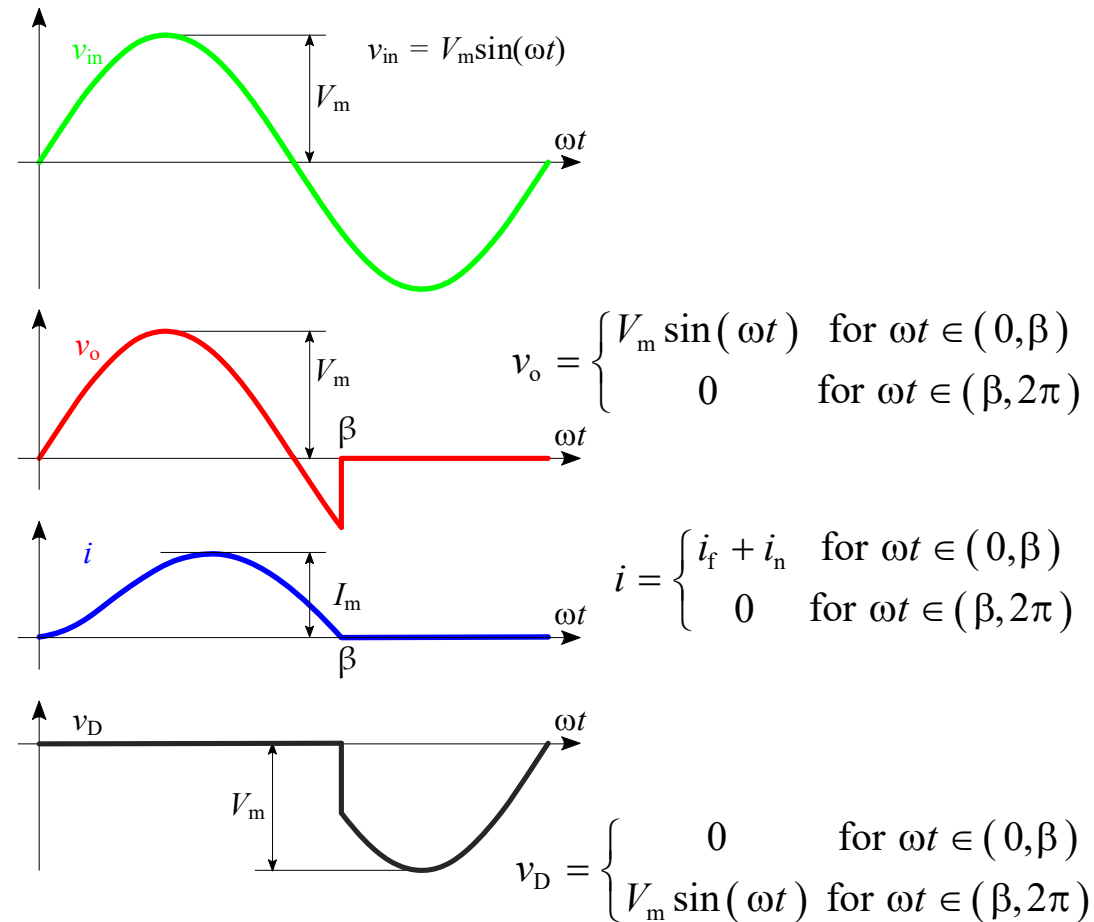
$$\text{where: } Z = \sqrt{R^2 + (\omega L)^2}; \varphi = \arctan\left(\frac{\omega L}{R}\right); \tau = \frac{L}{R}$$



Half wave rectifiers

The current i is composed of two components, the forced response i_f and natural response i_n .

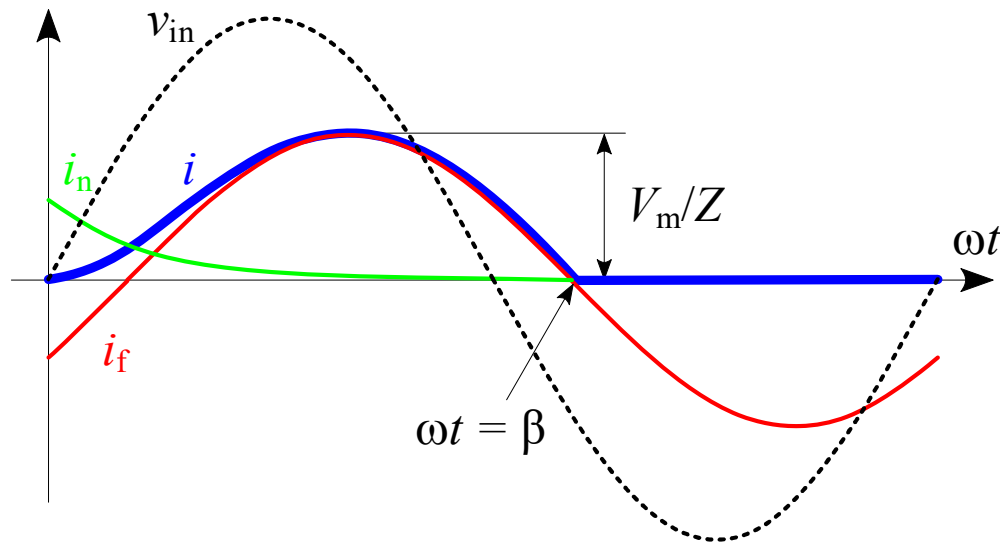
$$i = i_f + i_n = \underbrace{\frac{V_m}{Z} \sin(\omega t - \varphi)}_{i_f} + \underbrace{\frac{V_m}{Z} \sin(\varphi) e^{-\frac{t}{\tau}}}_{i_n}$$



The turn off angle β is required for calculating the average value of the output voltage and current. This angle can be numerically computed from the equation


$$i = 0 = \frac{V_m}{Z} \sin(\beta - \varphi) + \frac{V_m}{Z} \sin(\varphi) e^{-\frac{\beta}{\omega\tau}}$$
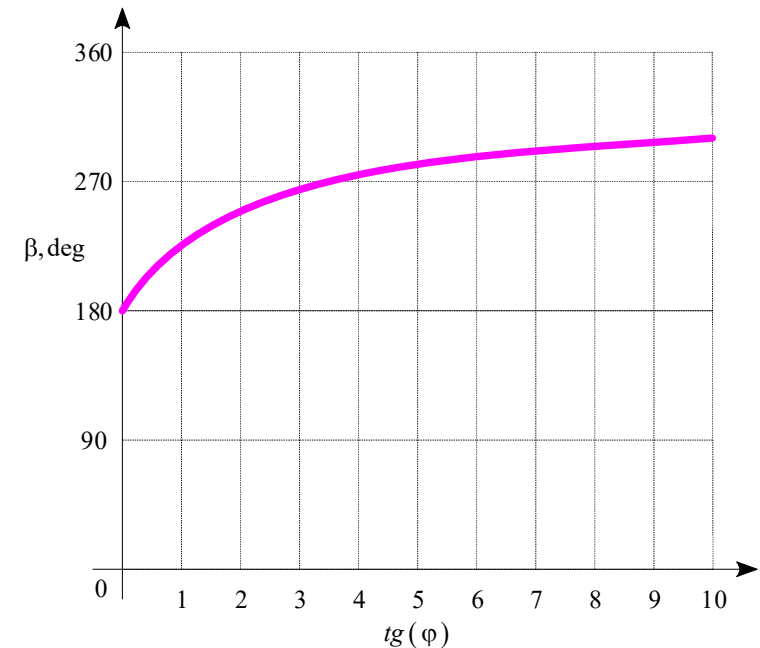
$$A \left[\sin(\beta - \varphi) + \sin(\varphi) e^{-\frac{\beta}{\omega\tau}} \right] = 0$$




Half wave rectifiers

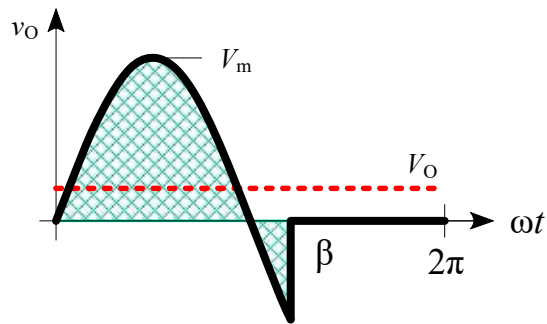The average value of the output voltage V_O for RL load is given as.



$$V_O = \frac{1}{2\pi} \int_0^\beta V_m \sin(\omega t) d\omega t = -\frac{V_m}{2\pi} \left[\cos(\omega t) \right]_0^\beta = \frac{V_m}{2\pi} [1 - \cos(\beta)]$$

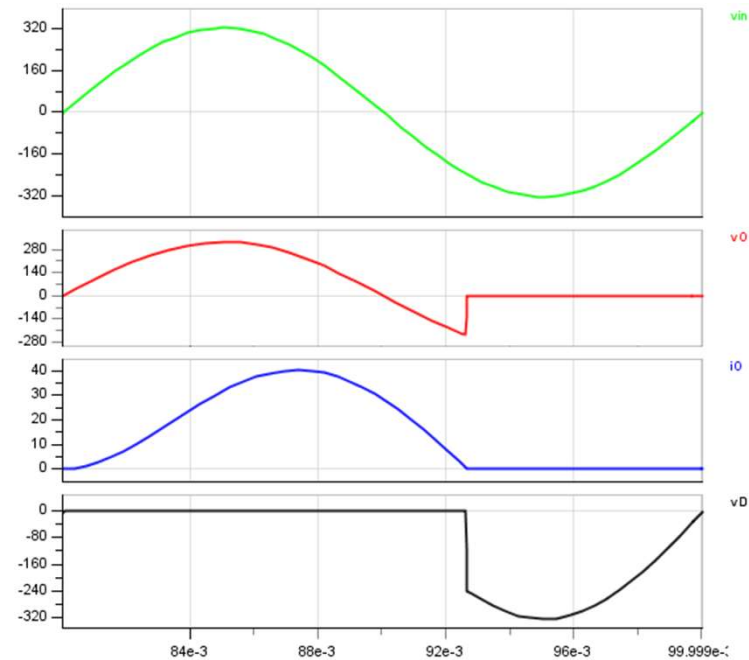Example of the diode half-wave diode rectifier with RL load ($R = 6 \Omega$, $L = 20 \text{ mH}$, $\text{tg}(\varphi) \approx 1$) supplied from sinusoidal voltage source $V_{\text{inrms}} = 230 \text{ V}$ ($V_m = 325 \text{ V}$).




Results

	avg	rms
vO	86.8288	170.7296
iO	14.4715	21.1915
vD	-86.8288	153.824
vin	-89.0743e-9	229.8053


Controlled half wave rectifiers

In the half-wave thyristor rectifier, the current i flows when thyristor is forward biased ($v_{in} > 0$) and to SCR gate current signal is applied.

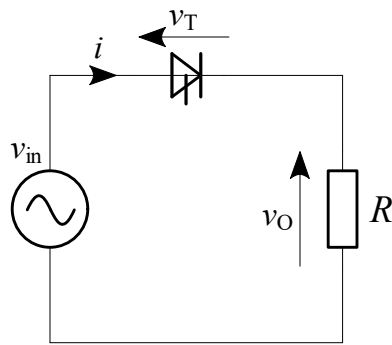The gate signal is applied synchronously with the fundamental period of v_{in} at the delay angle α .




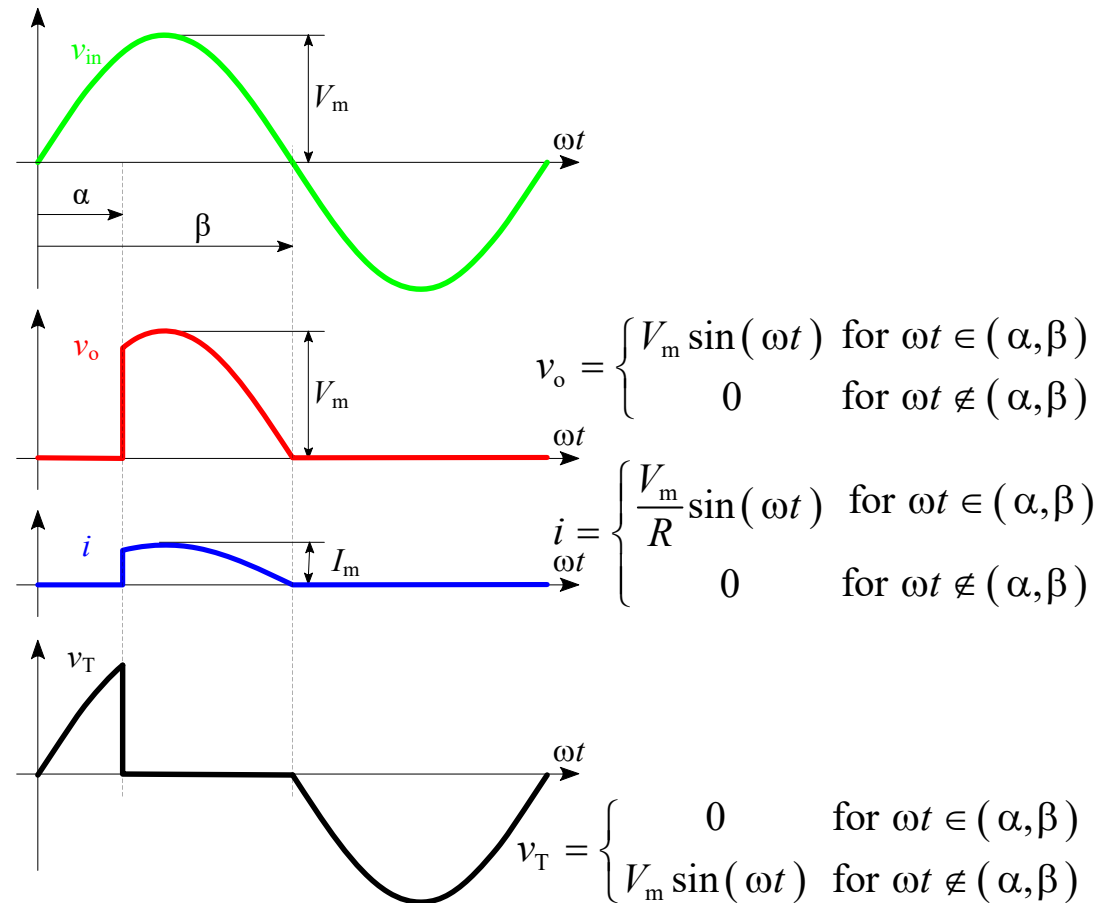In the half-wave thyristor rectifier with resistive load the turn-off angle $\beta = \pi$.



Controlled half wave rectifiers

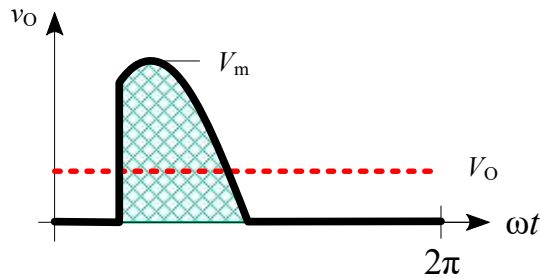The average value of the output voltage V_O of the half-wave thyristor rectifier with resistive load is given as




$$V_O = \frac{1}{2\pi} \int_{\alpha}^{\pi} V_m \sin(\omega t) d\omega t = -\frac{V_m}{2\pi} \left[\cos(\omega t) \right]_{\alpha}^{\pi} = \frac{V_m}{2\pi} \left[(1 + \cos(\alpha)) \right]$$

The average value of the current

$$I_{AV} = \frac{V_O}{R} = \frac{V_m}{2\pi R} \left[(1 + \cos(\alpha)) \right]$$

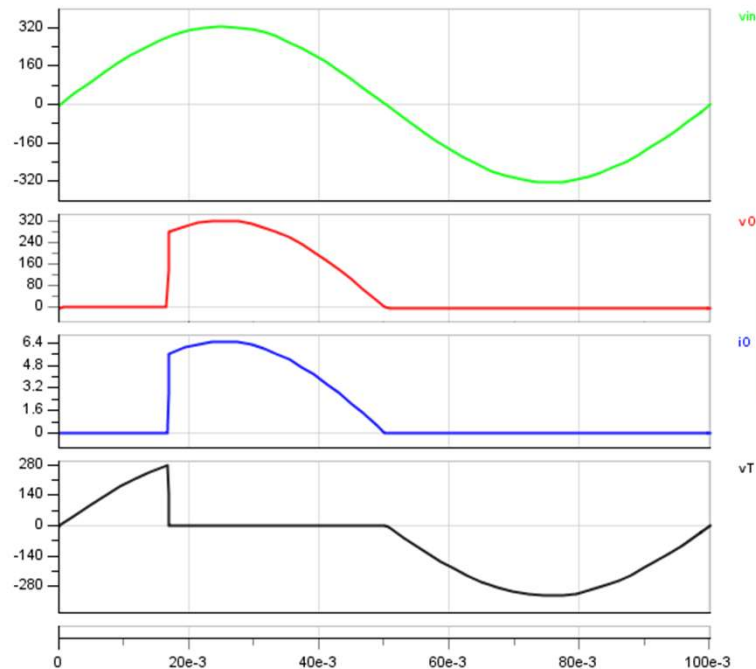Example of the thyristor half-wave diode rectifier with R load ($R = 50 \Omega$) supplied from sinusoidal voltage source $V_{inrms} = 230 \text{ V}$ ($V_m = 325 \text{ V}$) with a delay angle $\alpha = 60^\circ$.




Results

	avg	rms
vO	77.5694	145.719
iO	1.5514	2.9144
vT	-77.5694	177.6729
vG	50.0005e-3	223.6079e-3
vin	-89.0743e-9	229.8053


Controlled half wave rectifiers

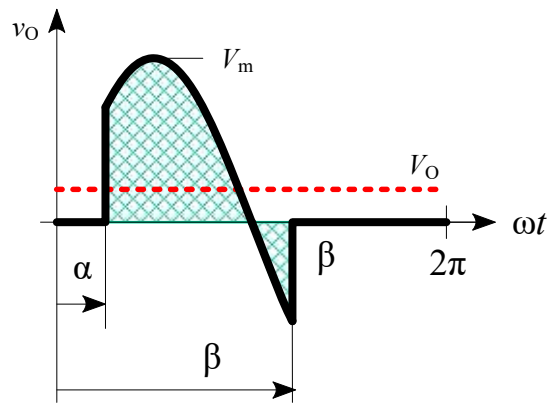The average value of the output voltage V_O of the half-wave thyristor rectifier with resistive-inductive load is given as



$$V_O = \frac{1}{2\pi} \int_{\alpha}^{\beta} V_m \sin(\omega t) d\omega t = -\frac{V_m}{2\pi} \left[\cos(\omega t) \right]_{\alpha}^{\beta} = \frac{V_m}{2\pi} [\cos(\alpha) - \cos(\beta)]$$

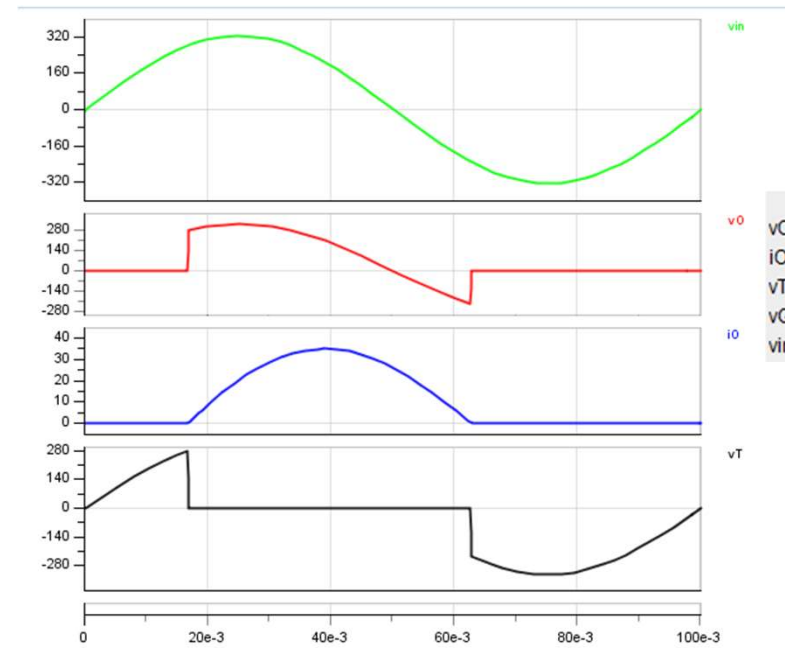Example of the diode half-wave thyristor rectifier with RL load ($R = 6 \Omega$, $L = 20 \text{ mH}$, $\text{tg}(\varphi) \approx 1$) supplied from sinusoidal voltage source $V_{\text{inrms}} = 230 \text{ V}$ ($V_m = 325 \text{ V}$) with a delay angle $\alpha = 60^\circ$.




Results

	avg	rms
vO	62.0667	153.8446
iO	10.3445	16.891
vT	-62.0667	170.6104
vG	50.0005e-3	223.6079e-3
vin	-89.0743e-9	229.8053



Half-wave rectifier

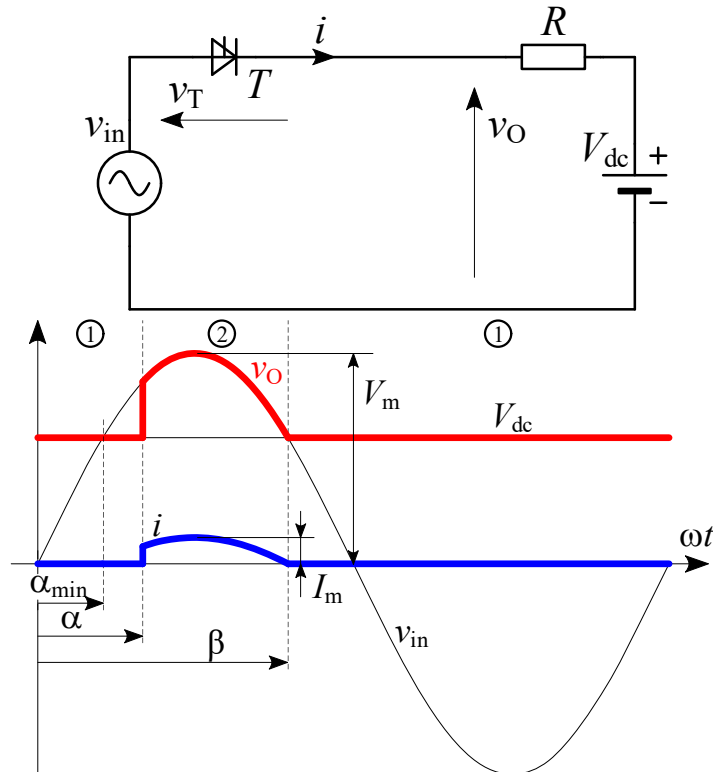Single-phase half-wave thyristor rectifier with RV_{dc} load



$$V_O = \frac{V_m}{2\pi} (\cos \alpha - \cos \beta) + V_{dc} \left(1 - \frac{\beta - \alpha}{2\pi} \right)$$

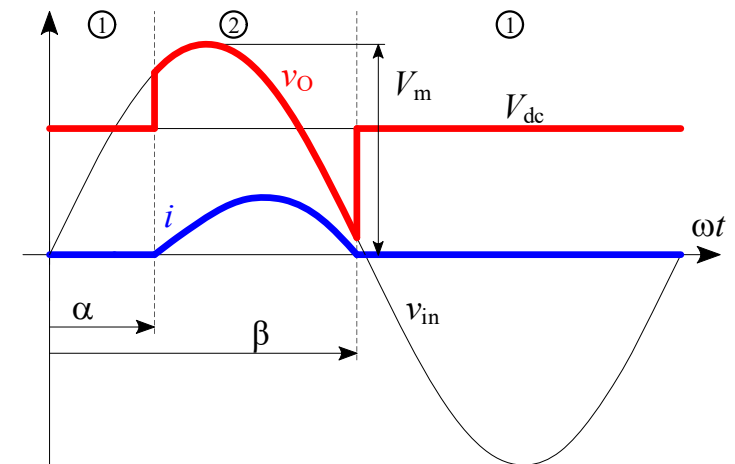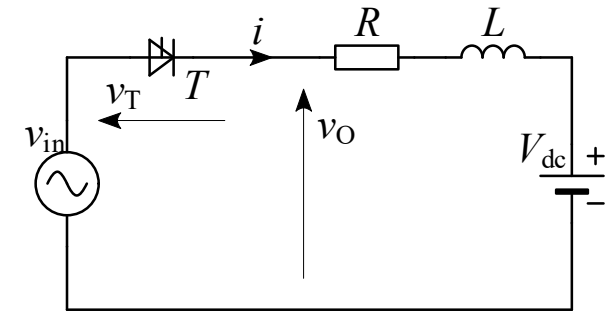
Single-phase half-wave thyristor rectifier with RLV_{dc} load



$$V_O = \frac{V_m}{2\pi} (\cos \alpha - \cos \beta) + V_{dc} \left(1 - \frac{\beta - \alpha}{2\pi} \right)$$


Full-wave rectifier

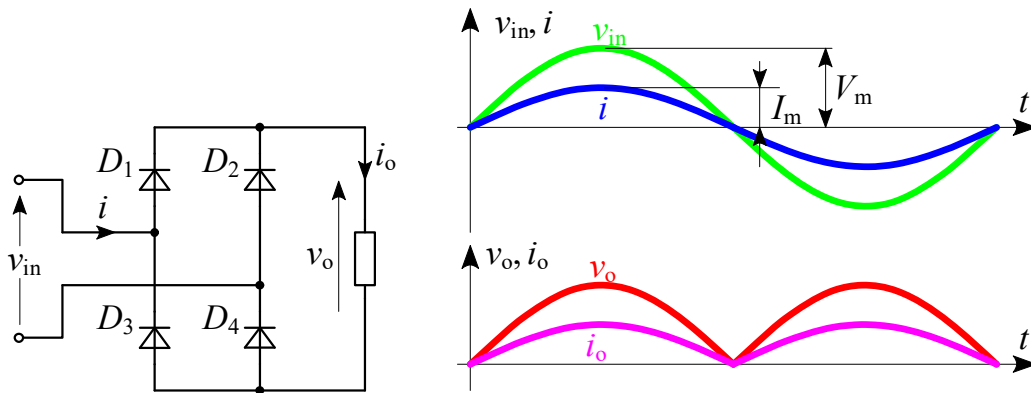Single-phase full-wave diode rectifier with R load



$$V_O = \frac{1}{\pi} \int_0^{\pi} V_m \sin(\omega t) d\omega t = \frac{2V_m}{\pi}$$

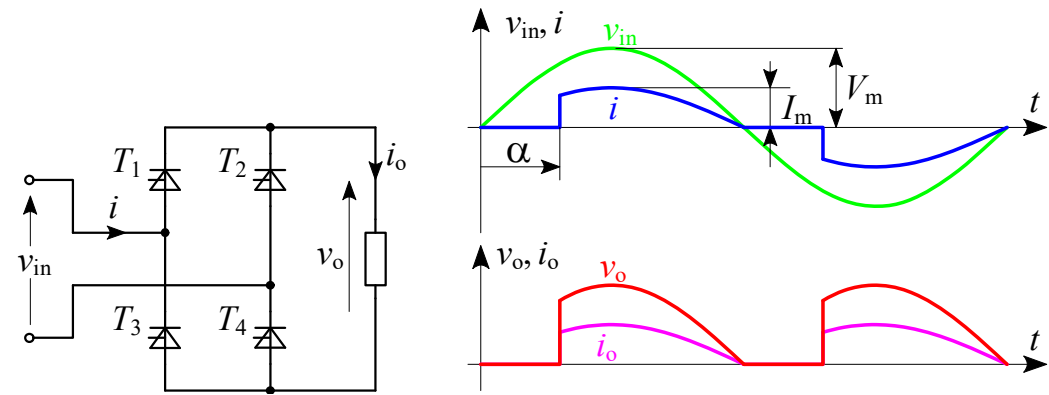
Single-phase full-wave thyristor rectifier with R load



$$V_O = \frac{1}{\pi} \int_{\alpha}^{\pi} V_m \sin(\omega t) d\omega t = \frac{V_m}{\pi} [(1 + \cos(\alpha))]$$

Full-wave rectifier RL

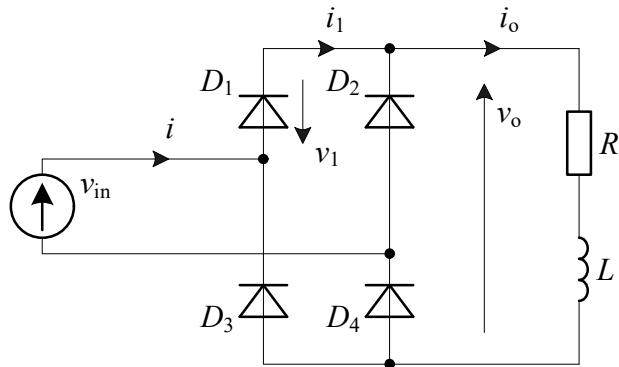
Single-phase full-wave diode rectifier with RL load



Load current could be constant with limited ripple



The full-wave bridge rectifier can operate in CCM with RL load

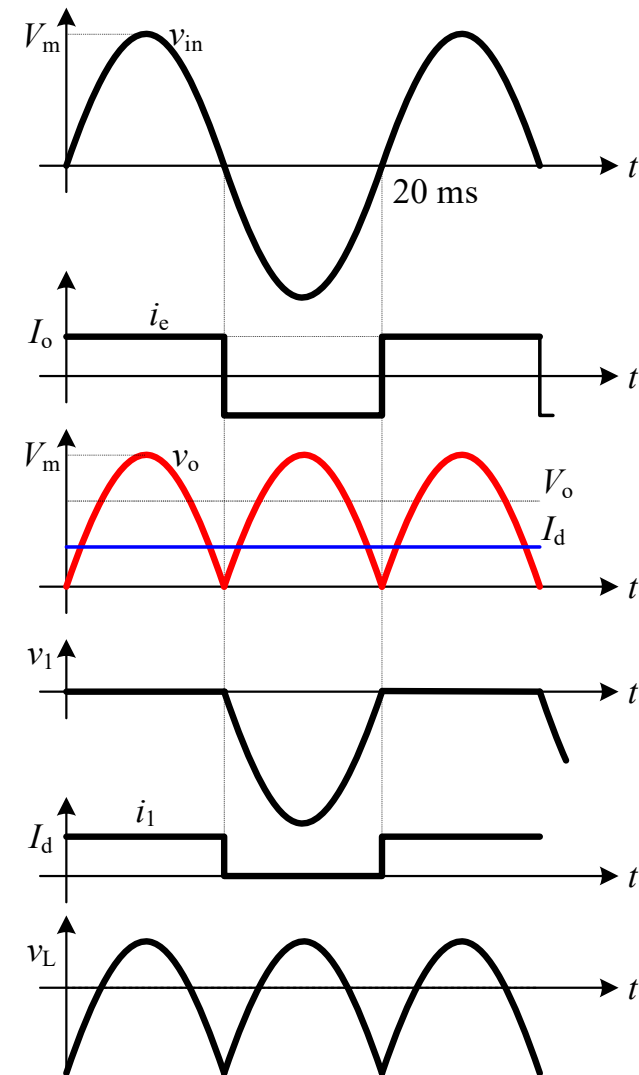RL load is limited to DC drive systems, welding machines, electrolysis reactors



Full-wave rectifier RC

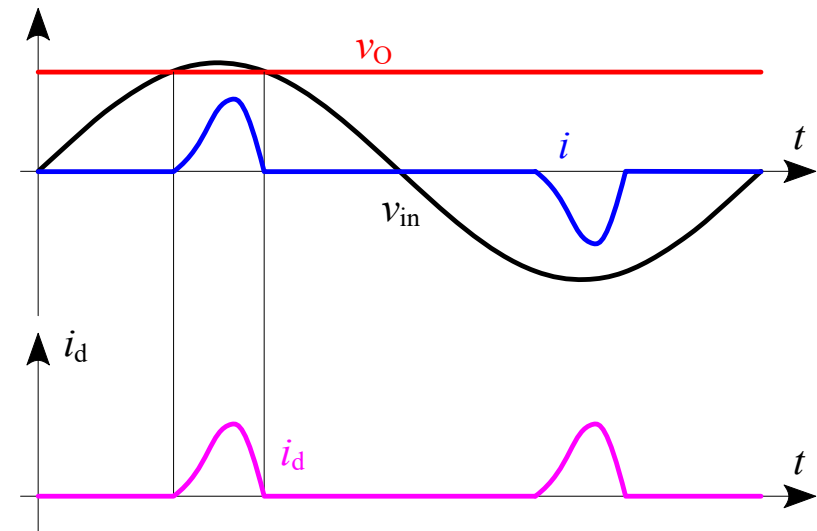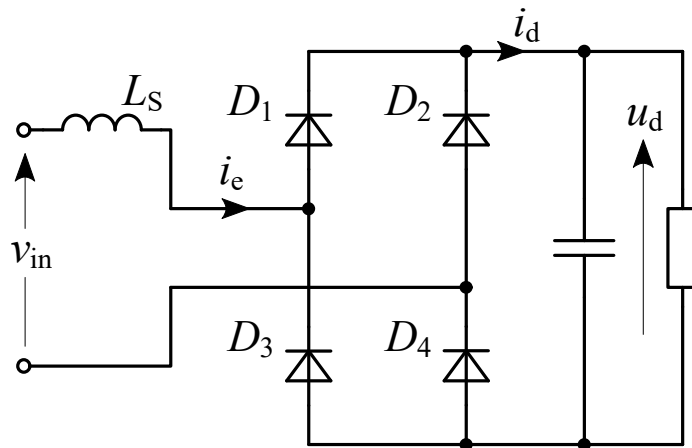Single-phase full-wave diode rectifier with RC load



Load current is not continuous thus converter always operates in DCM.


Conduction angles depend on RLC parameters and phase currents can be more distorted than currents of rectifiers with RL loads.

RC load is commonly used in domestic low power appliances and medium and high-power adjustable drive systems.


Six-pulse rectifiers

Three-phase full-wave rectifiers are also known as six-pulse rectifiers. There are similar options of rectifiers as for half-wave rectifiers or single-phase rectifiers.

Six-pulse diode rectifier with RL load

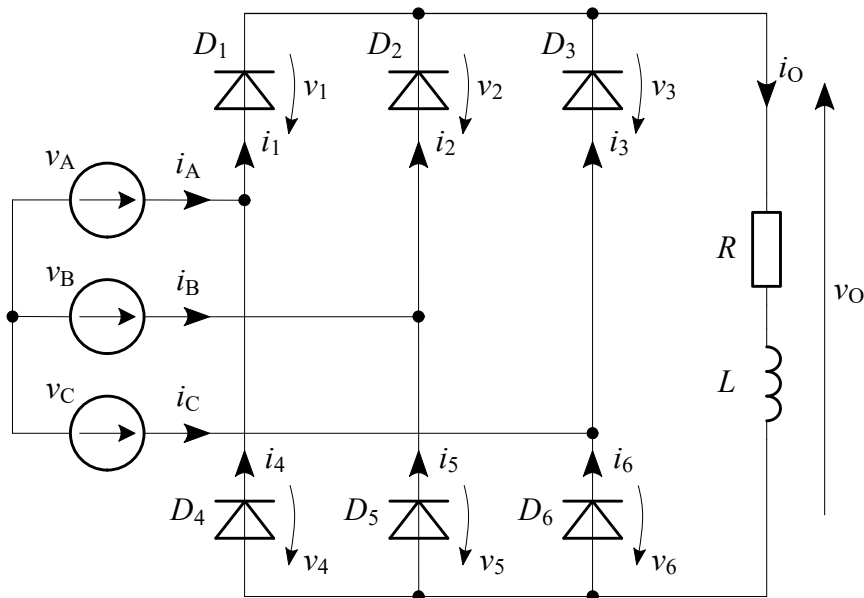


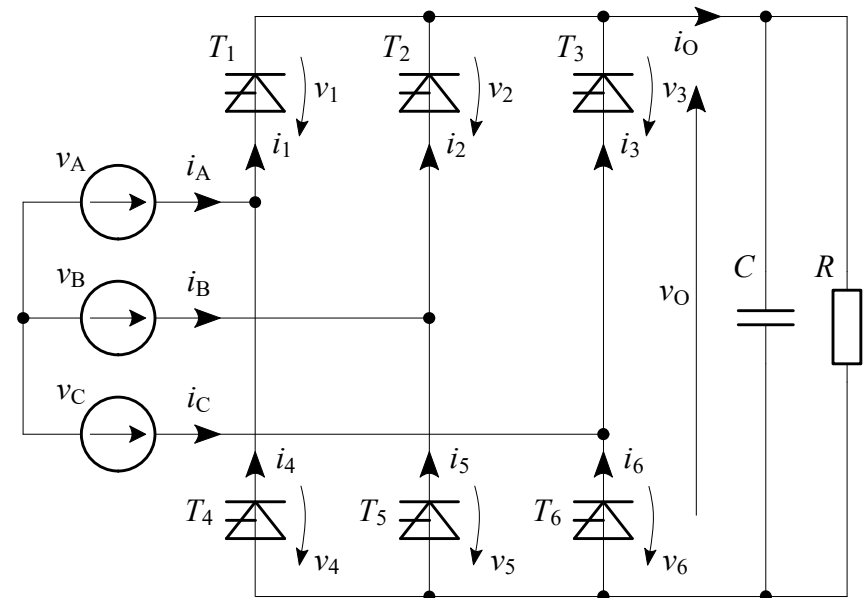Six-pulse thyristor rectifier with RC load




Six-pulse diode rectifier – output voltage

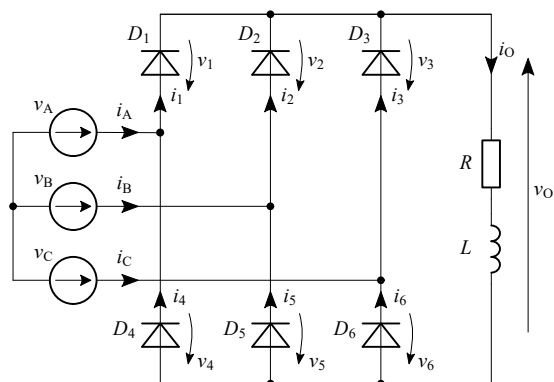The operation of six-pulse diode rectifier with continuous output current i_O .




There are 6 equivalent circuits

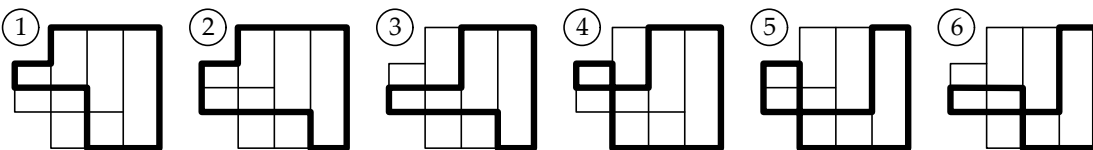

At the same time only two diodes conduct current. One diode is from upper group (D_1, D_2, D_3) and the second is from lower group (D_4, D_5, D_6)

Output voltage

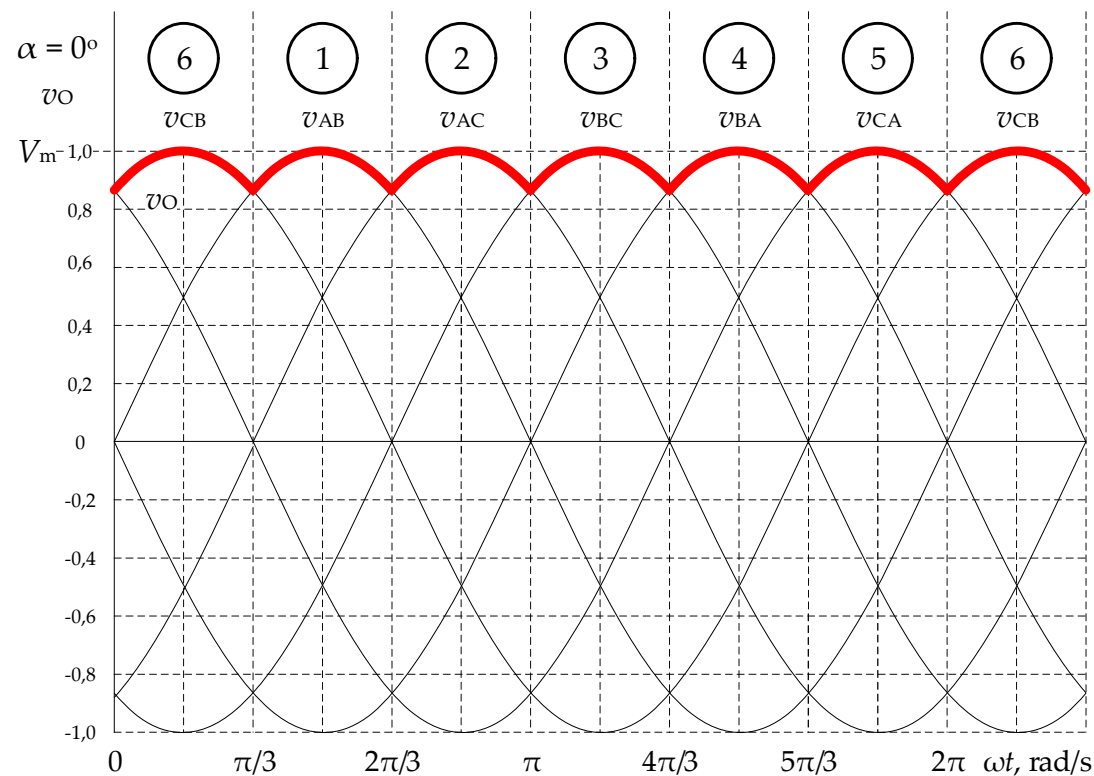


Six-pulse diode rectifier

The average value of the output voltage of the six-pulse rectifier is calculated as

$$V_O = \frac{1}{2\pi} \cdot 6 \cdot \int_{\frac{\pi}{3}}^{\frac{2\pi}{3}} V_m \sin(\omega t) d\omega t = \frac{6V_m}{2\pi} \left(\cos\left(\frac{\pi}{3}\right) - \cos\left(\frac{2\pi}{3}\right) \right) =$$

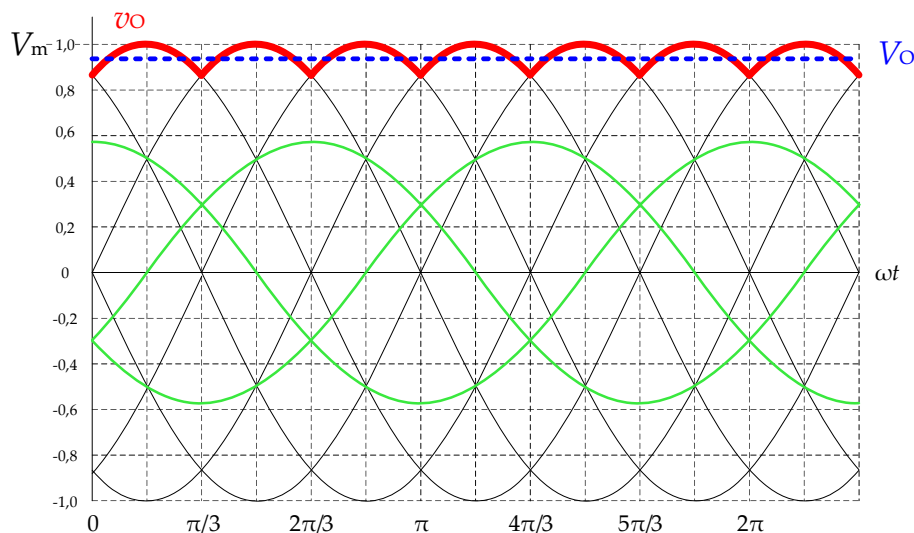
$$= \frac{6V_m}{2\pi} \left(\frac{1}{2} + \frac{1}{2} \right) = \frac{3V_m}{\pi}$$



In general q -pulse rectifiers the average value of the output voltage

$$V_O = \frac{q}{2\pi} \int_{\frac{\pi}{2} - \frac{\pi}{q}}^{\frac{\pi}{2} + \frac{\pi}{q}} V_m \sin(\omega t) d(\omega t) = \frac{qV_m}{2\pi} \left(-\cos(\omega t) \right) \Big|_{\frac{\pi}{2} - \frac{\pi}{q}}^{\frac{\pi}{2} + \frac{\pi}{q}} =$$
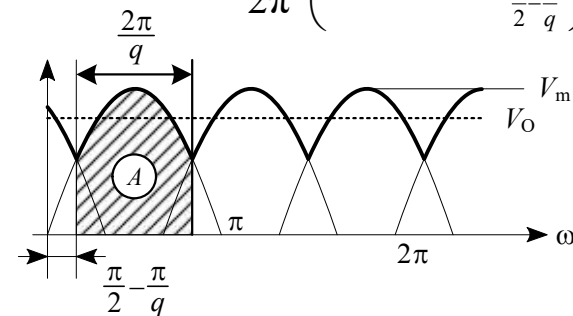
$$= \frac{qV_m}{\pi} \sin\left(\frac{\pi}{q}\right)$$




In the half-wave rectifiers V_m is an amplitude of the phase voltage, but in full-wave rectifiers V_m is an amplitude of the line-to-line voltage.

For 6-pulse rectifier supplied from three-phase grid with line-to-line voltage $V_{ll,rms} = 400$ V the output voltage is:


$$V_O = \frac{6V_m}{\pi} \sin\left(\frac{\pi}{6}\right) \stackrel{V_m = \sqrt{2} \cdot 400V}{=} \frac{3\sqrt{2} \cdot 400V}{\pi} = 540.2$$

Six-pulse diode rectifier – diode voltage

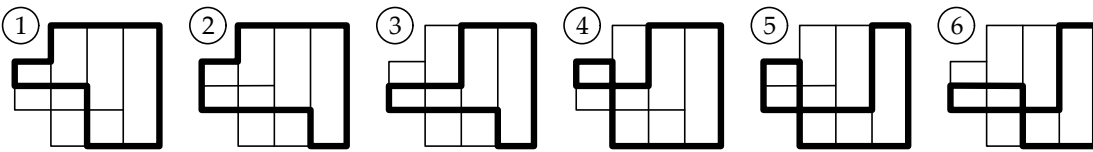
The diode voltages in different equivalent circuits are composed of different line-to-line voltages



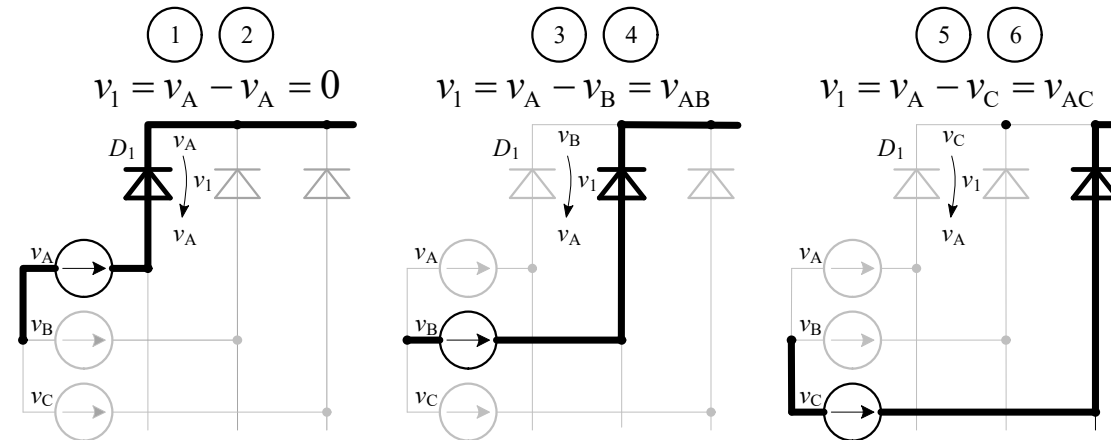The diode D_1 voltage v_1 is a difference of the anode and the cathode voltages.




Diode D_1 voltage v_1 in CCM

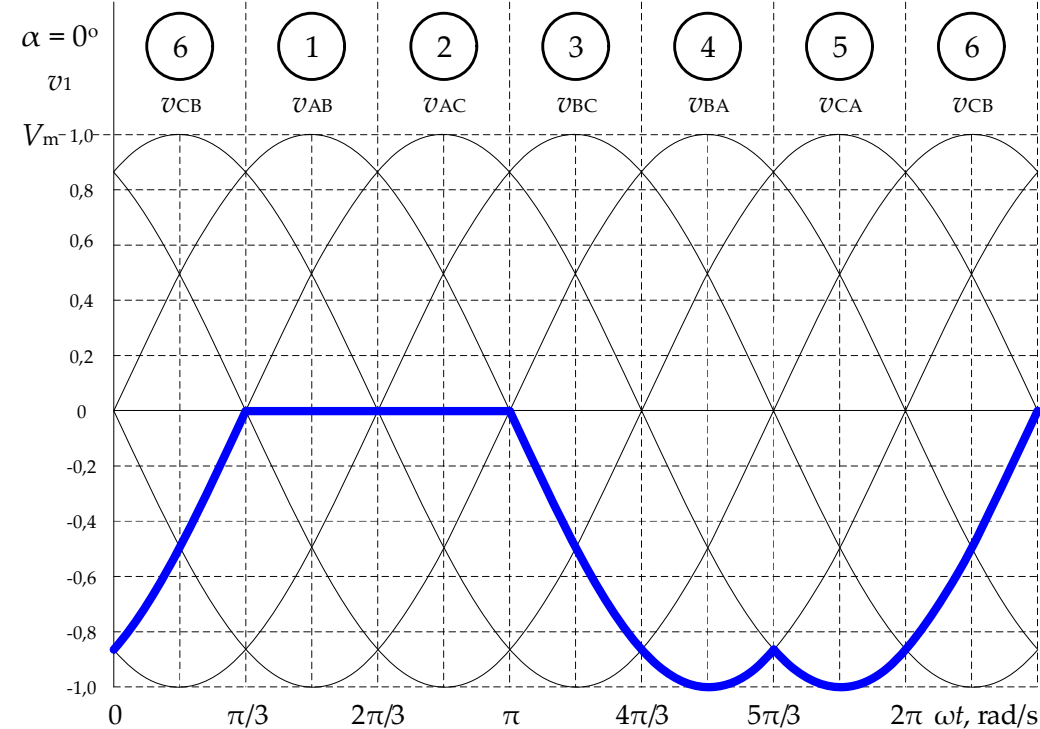

Voltages across other diodes are similar to v_1 but phase-shifted by multiple of 60°

Six-pulse diode rectifier – current waveforms

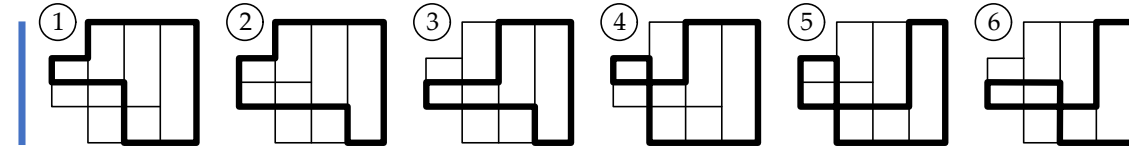Output current in the six-pulse diode rectifier depends on the load type and its parameters.






load type

output current i_o




diode D_1 and D_4 currents

phase A current i_A

R

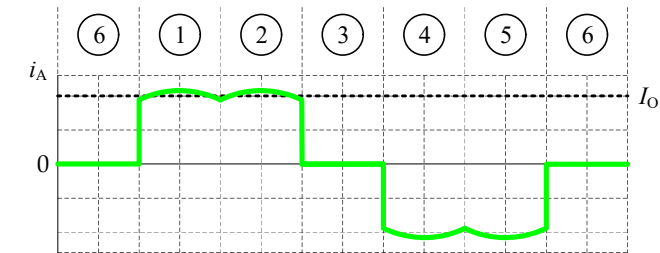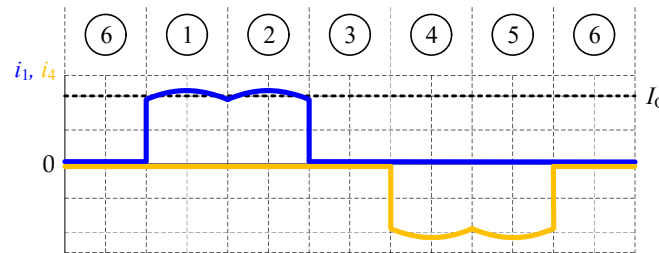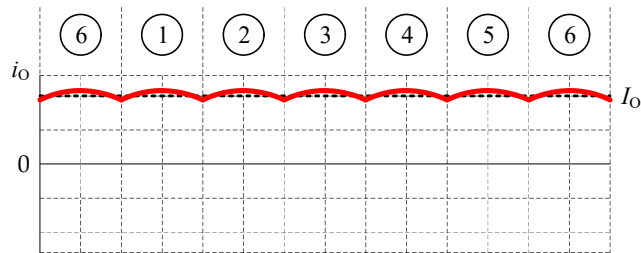

RL

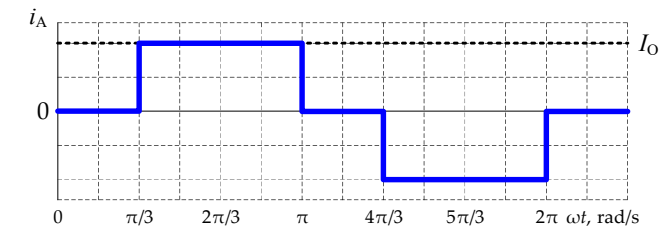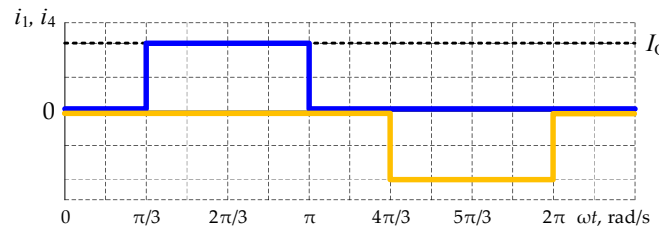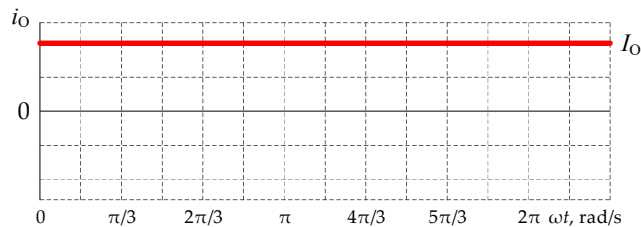

The rectifier currents are calculated from:

$$I_o = \frac{V_o}{R}$$


$$I_{1AV} = \frac{1}{3} I_o$$

$$I_{AAV} = 0$$

Six-pulse diode rectifier – phase current harmonic spectrum

Phase current i_A consists of harmonic components I_{Ah}
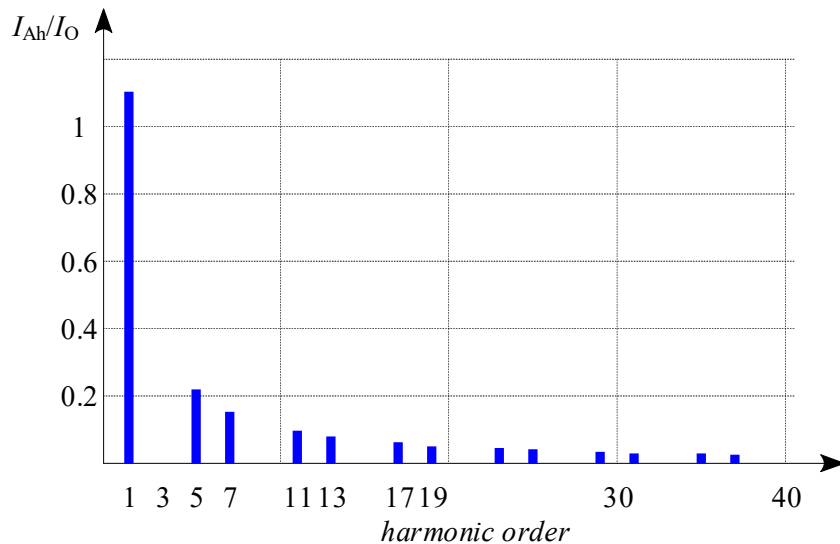
$$I_{Ah} = \begin{cases} \frac{4}{\pi} \frac{I_O}{h} \cos\left(h \frac{\pi}{6}\right) & \text{for odd harmonics} \\ 0 & \text{for even harmonics} \end{cases}$$



Only odd harmonics which are not multiples of three exist in the phase current ($h = k \times 6 \pm 1$)

The amplitude of the phase current fundamental component I_{A1} is transferring active and reactive power.

$$I_{A1} = \frac{4}{\pi} I_O \frac{\sqrt{3}}{2} = \frac{2\sqrt{3}}{\pi} I_O$$

The output power P_O is

$$P_O = I_O V_O = \frac{3}{\pi} I_O V_m = \frac{3\sqrt{2}}{\pi} I_O V_{ll}$$


The input power P_{in} of the three-phase six-pulse rectifier

$$P_{in} = \sqrt{3} \frac{I_{A1}}{\sqrt{2}} V_{ll} = \sqrt{3} \frac{2\sqrt{3}}{\sqrt{2}\pi} I_O V_{ll} = \frac{3\sqrt{2}}{\pi} I_O V_{ll}$$


The input power P_{in} is equal to the output power because it is assumed that rectifier is lossless.

Six-pulse diode rectifier – RC load

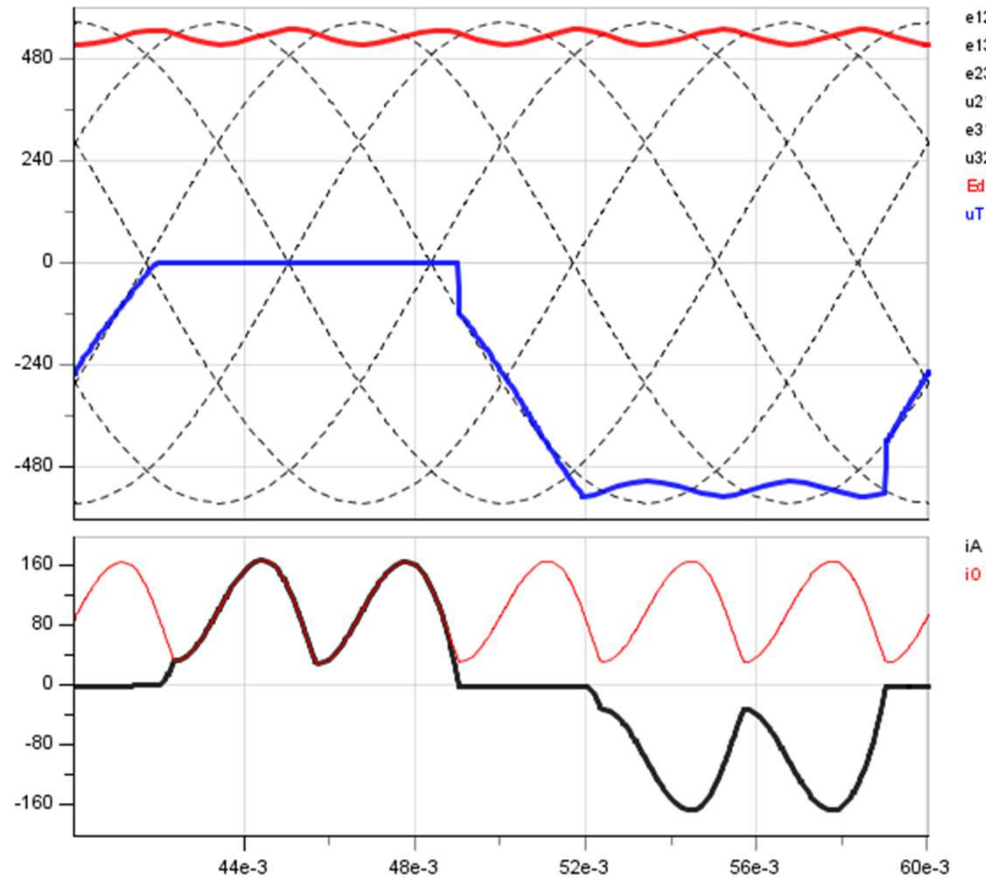The six-pulse rectifier with RC load operating in CCM




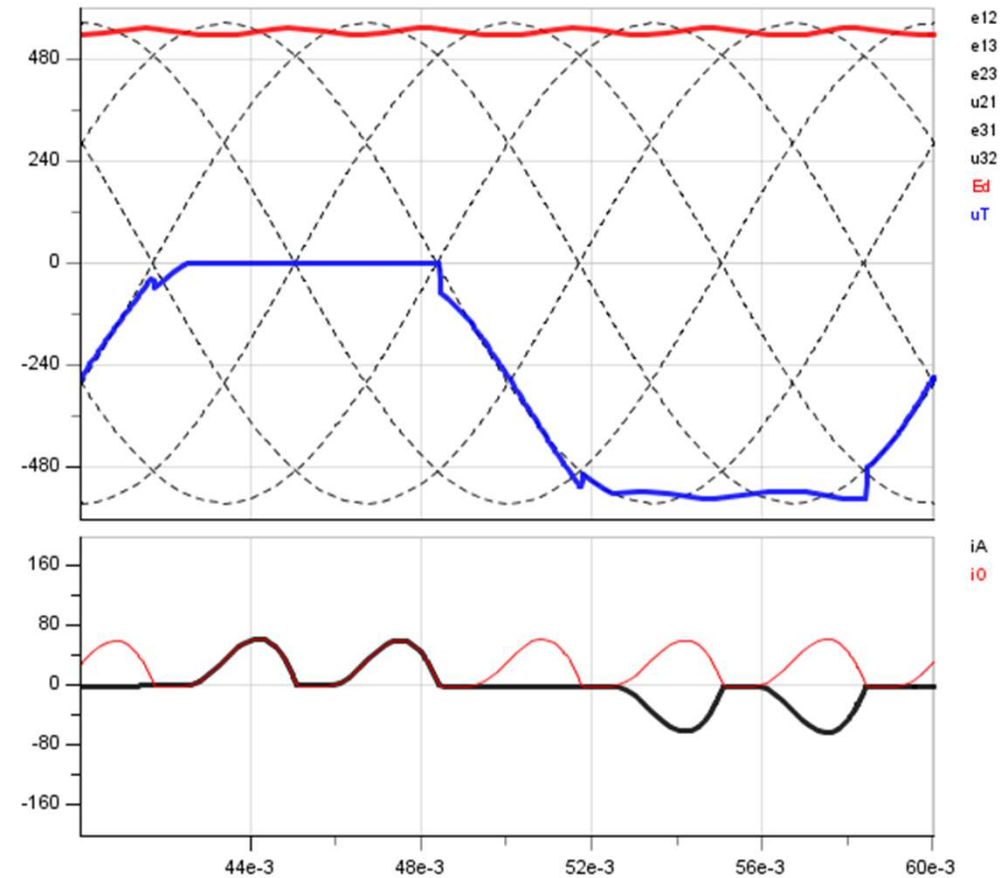The six-pulse rectifier with RC load operating in DCM




Six-pulse thyristor rectifier – output voltage

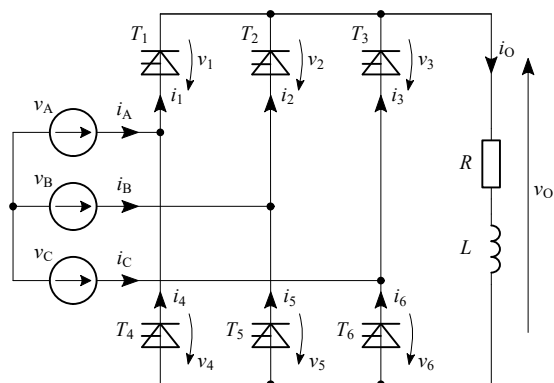The operation of six-pulse thyristor rectifier with continuous output current i_O .




Thyristors are turned on with a delay angle α .

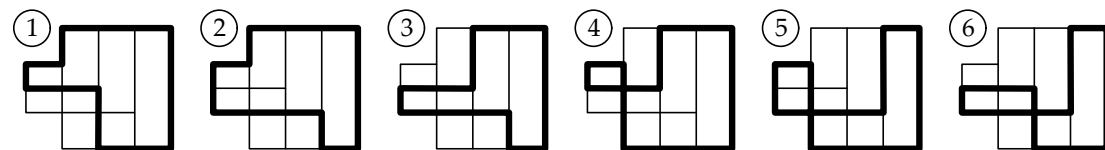All 6 equivalent circuits are the same as in the six-pulse diode rectifier




Output voltage

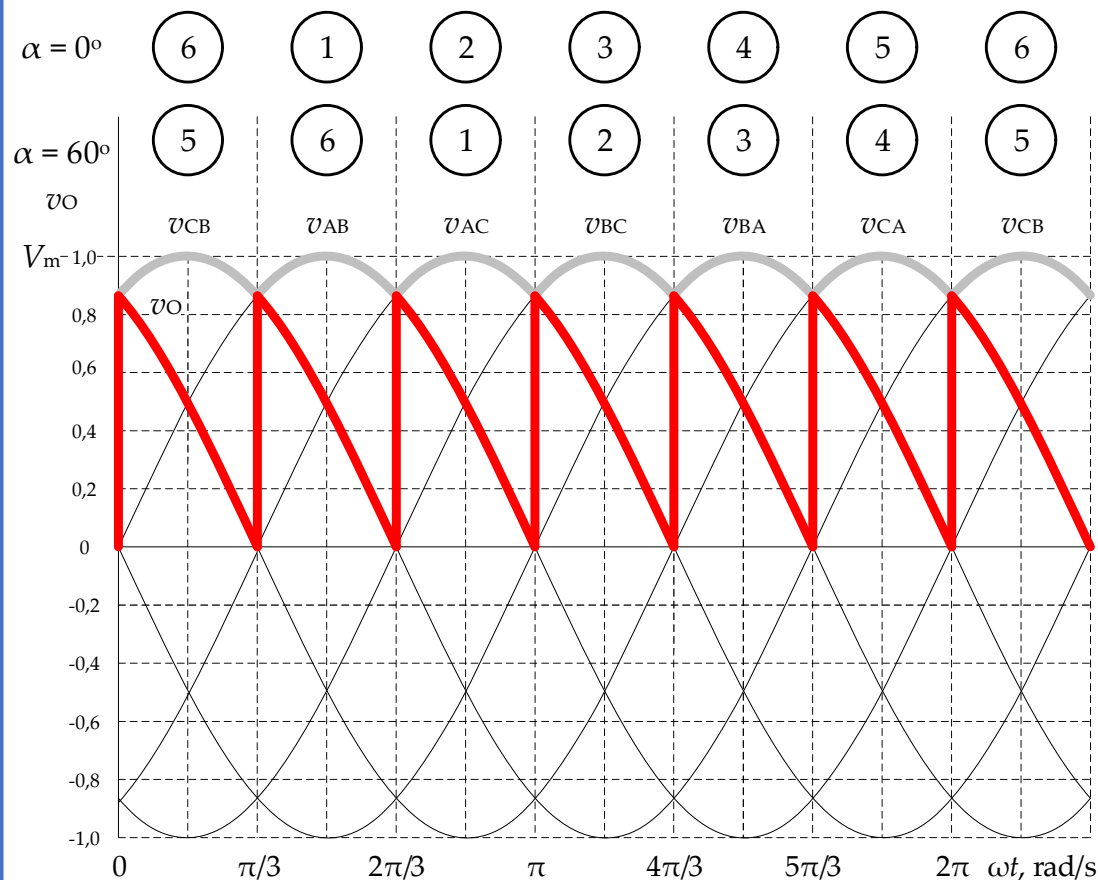


Six-pulse thyristor rectifier – output voltage

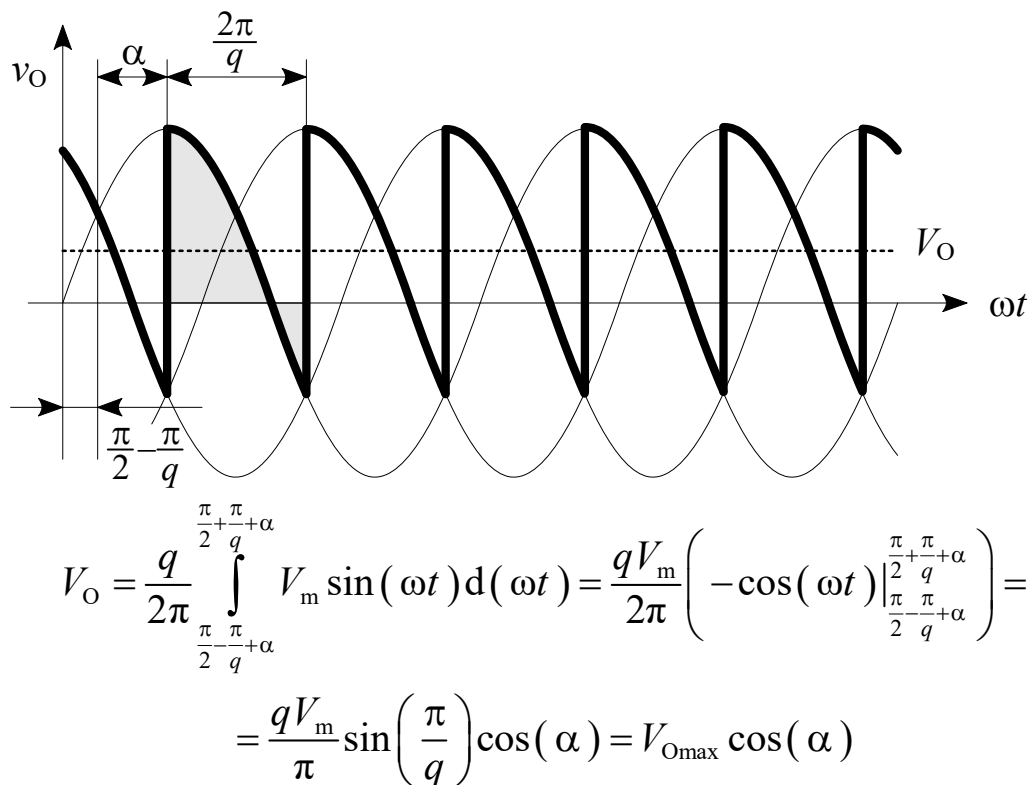The average value of the output voltage V_O depends on the delay angle α .



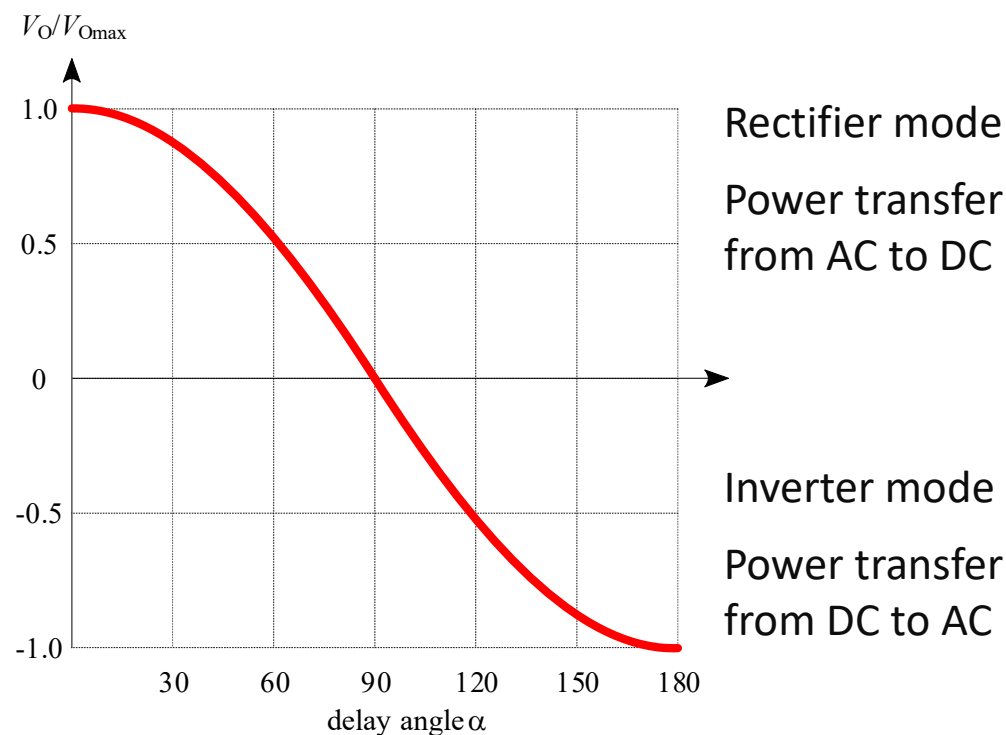
The output current flows only in one direction but the average value of the output voltage V_O can be with both polarities.




Six-pulse thyristor rectifier – constant output current

The delay angle $\alpha = 90^\circ$


The output voltage

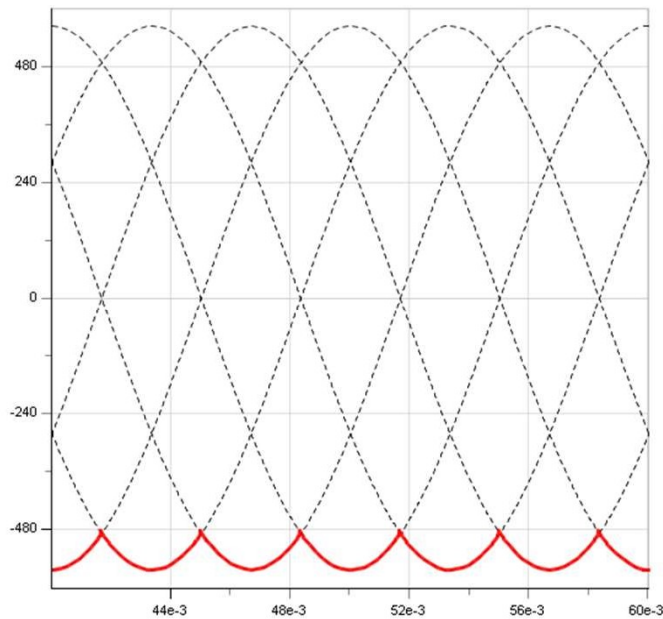

The thyristor T_1 voltage

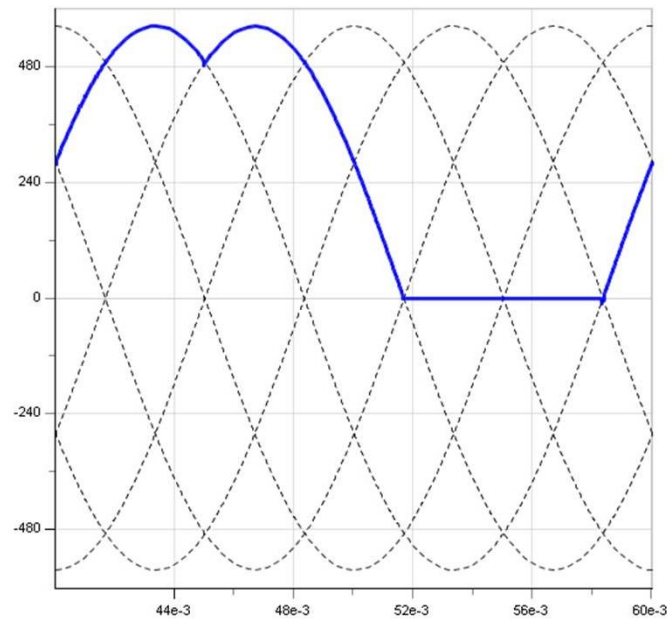

The phase and thyristor currents

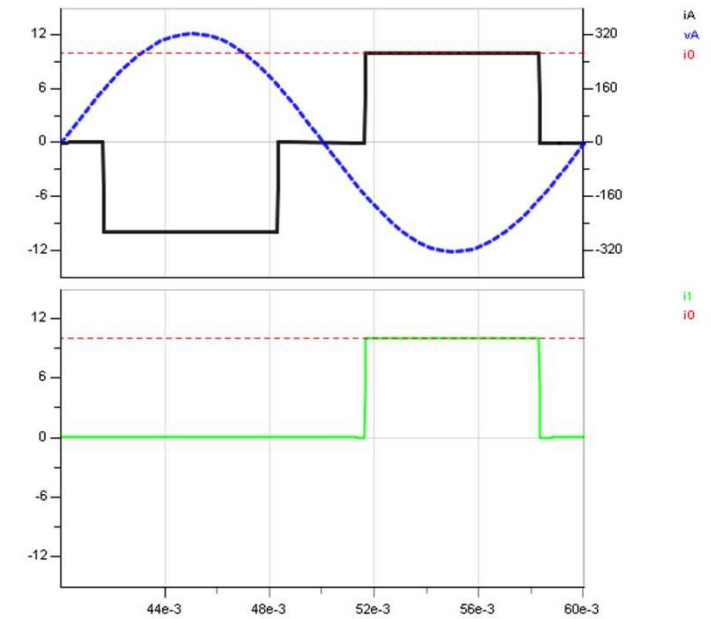

Six-pulse thyristor rectifier – the operation with high α

The load which acts as a constant output current source can occur only in specific applications:

- Electrical drive systems with dc machines
- **H**igh **V**oltage **D**irect **C**urrent Transmission Systems HVDC.


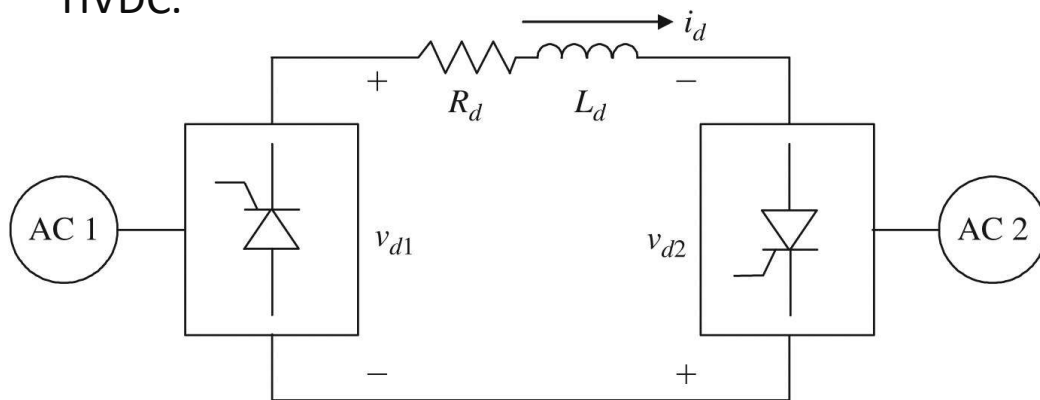


Figure 13.14
© John Wiley & Sons, Inc. All rights reserved.


The power flow depends on voltage polarisation only because the current is unidirectional.

The output voltage characteristic $V_O = f(\alpha) = V_{Omax} \cos \alpha$ is only for CCM operation. For converters with R or RL loads DCM when $\alpha > 60^\circ$

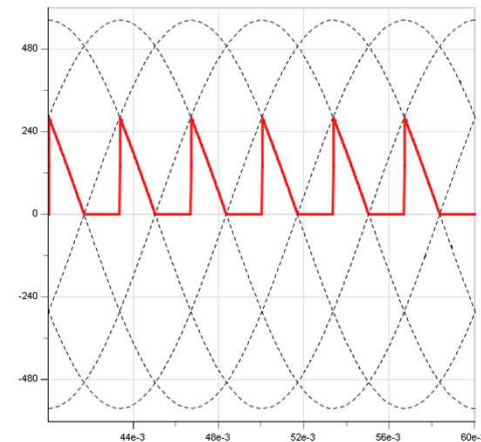The output voltage for R load with $\alpha = 90^\circ$






The output voltage characteristic

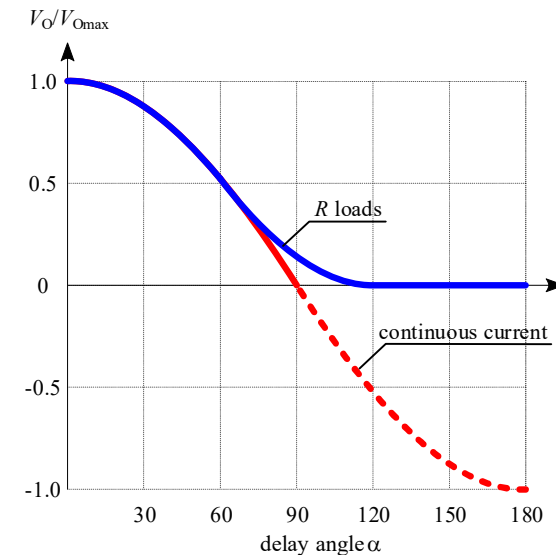

Six-pulse thyristor rectifier – commutation

Why are thyristors or diodes switched off when they were conducting?

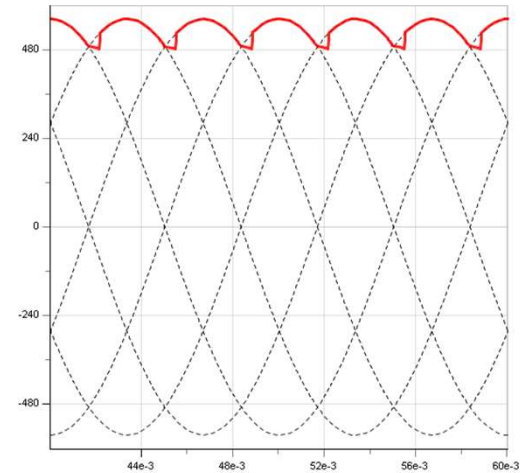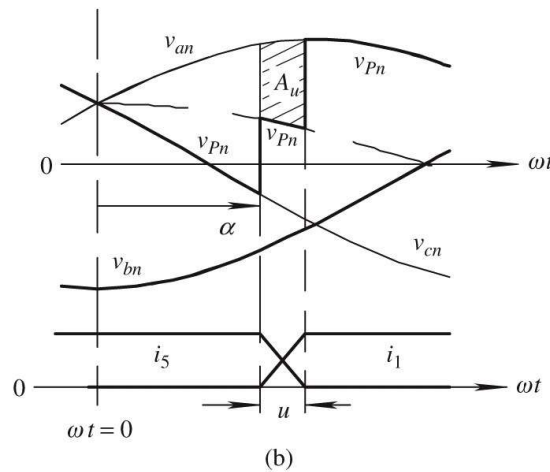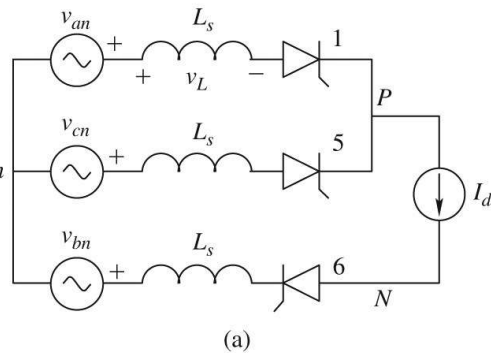A: Other diodes from the same group form a fast-passing short-circuit lasting until the current in new diode is equal i_o (the current in previously conducting diode reaches zero).



$$V_O = \frac{3}{\pi} V_m - \Delta V_{\text{com}}$$

$$\Delta V_{\text{com}} = \frac{3}{\pi} I_d L_S$$


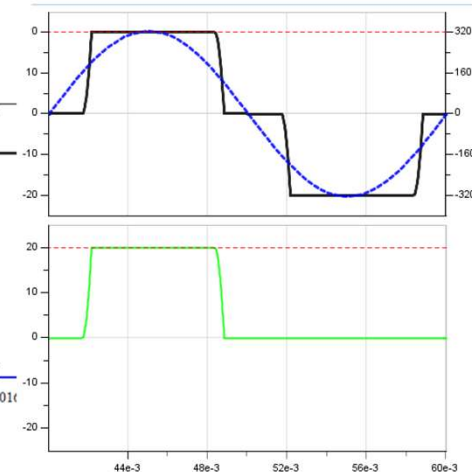
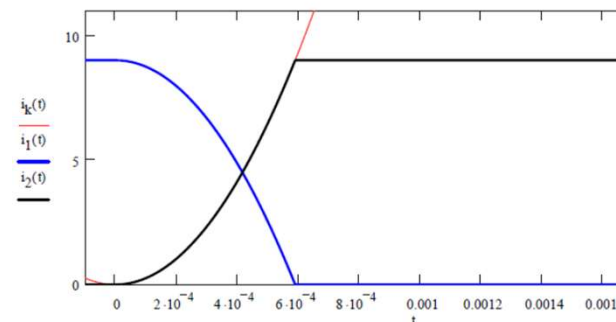
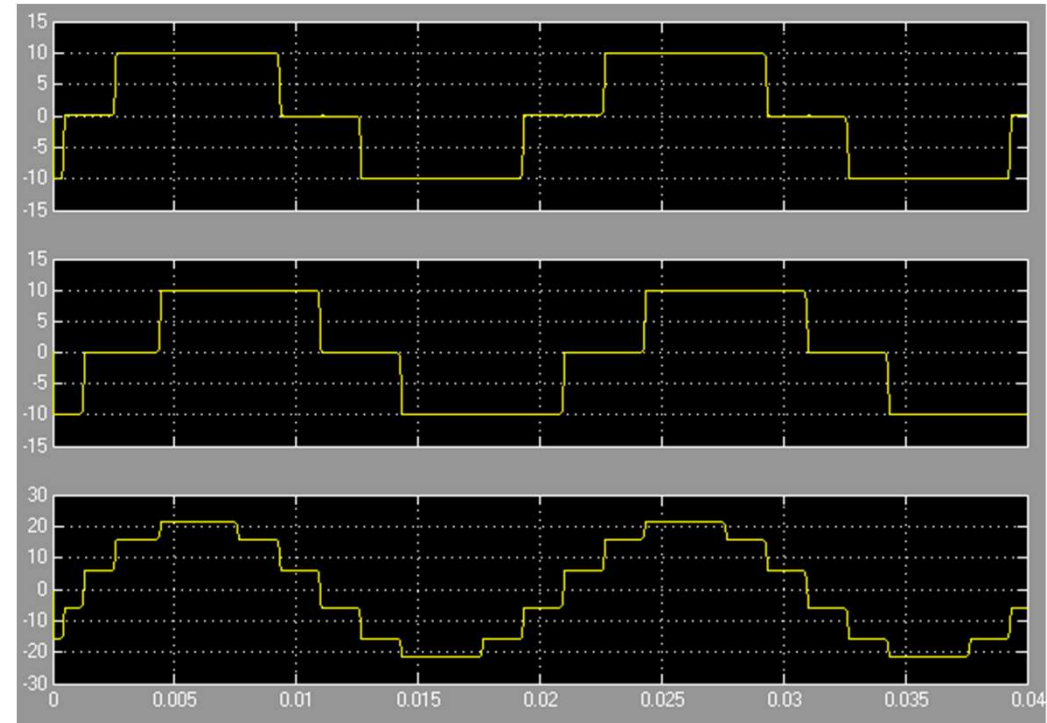


Figure 13.12
© John Wiley & Sons, Inc. All rights reserved.

Multipulse rectifiers

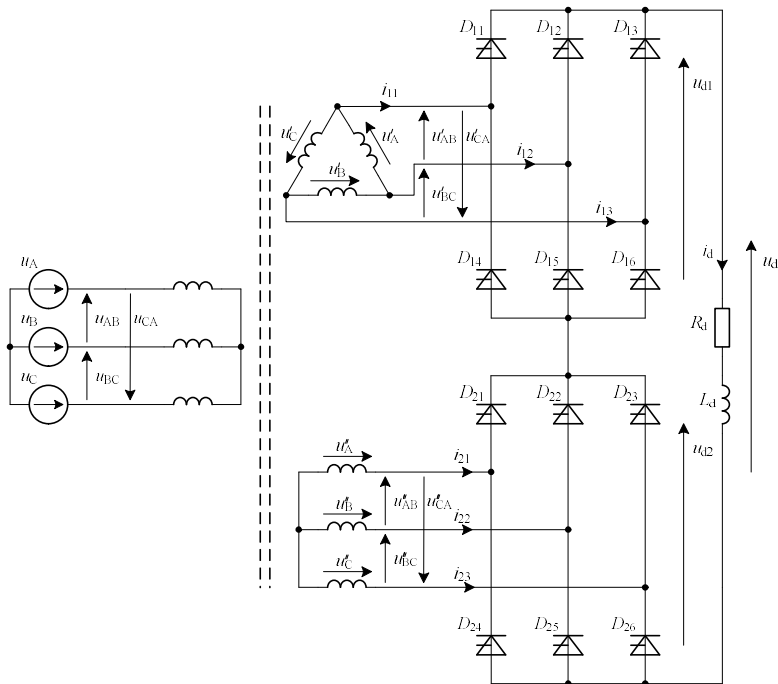Twelve pulse rectifier is constructed from two six-pulse rectifiers which outputs are connected in series, but supply voltages are separated by using transformers producing phase shifted voltage by 30°



In the phase current of the 12-pulse rectifier the following harmonics exist $h = 11, 13, 23, 25...$
($h = k \times 12 \pm 1$)